


Cascaded Noise-Shaping Modulators for Oversampled Data Conversion

Bruce A. Wooley
Stanford University



Outline

- **Oversampling modulators for A/D conversion**
- **Cascaded noise-shaping architectures**
- **Embedded quantization**
- **Distributed noise shaping zeros**
- **Bandpass cascaded modulator**
- **Digital cascaded modulators with semi-digital reconstruction for D/A conversion**



Analog-to-Digital Conversion

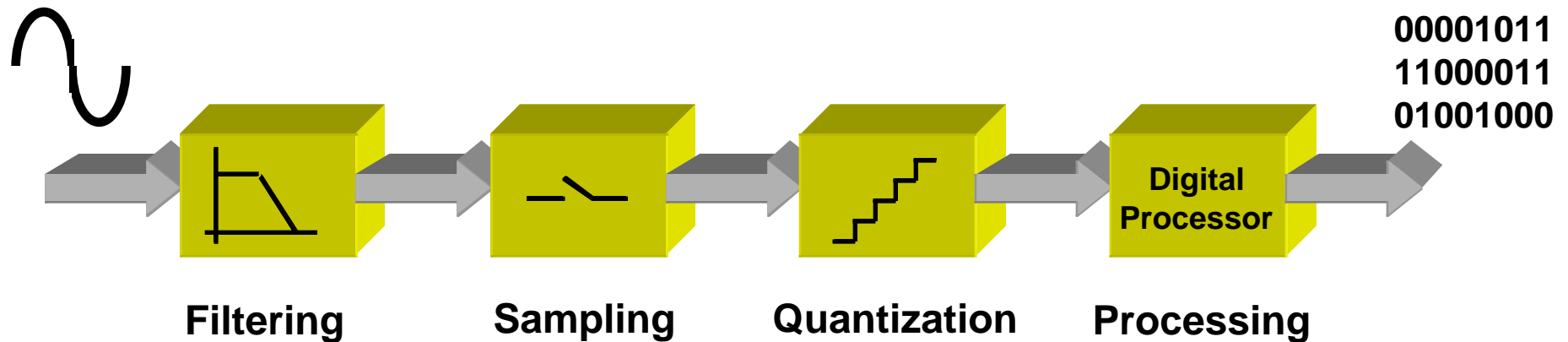



Quantization Model:

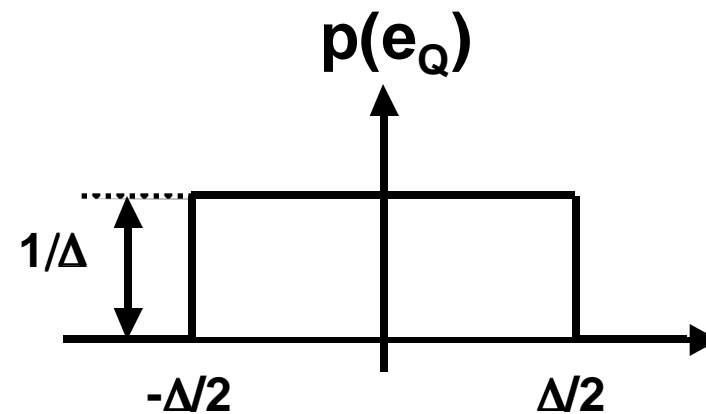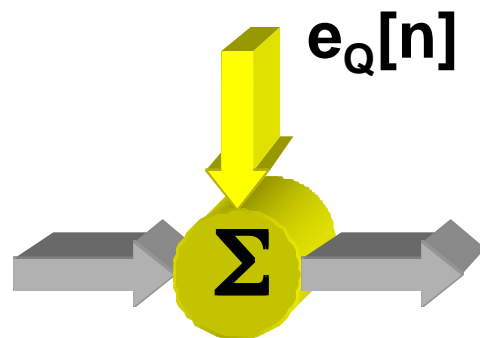

Noise Shaping

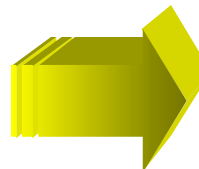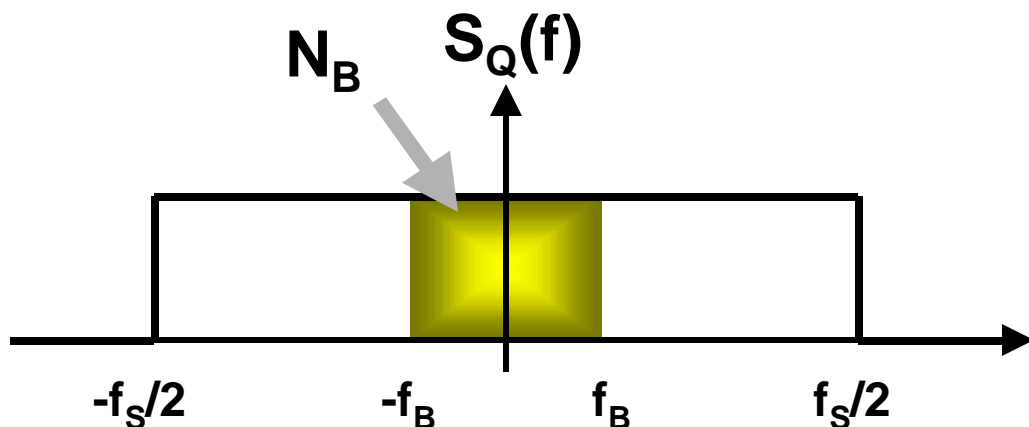

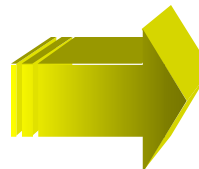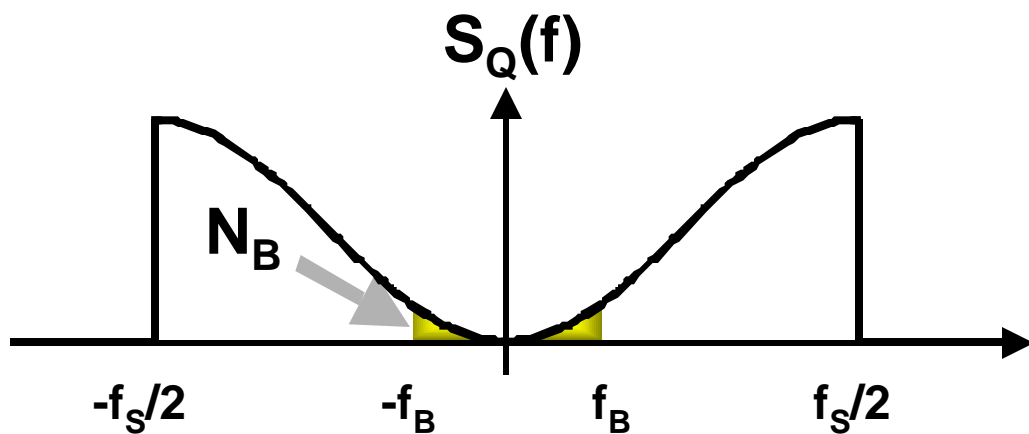Quantizer resolution
increased by 3 dB
per octave of
OVERSAMPLING




Quantizer resolution
increased through
NOISE SHAPING

Oversampling Modulators


- **Embed quantizer in a feedback loop to achieve larger improvement in resolution with increasing M**
- **Feedback used for PREDICTION (Δ Modulation) or NOISE SHAPING ($\Sigma\Delta$ Modulation)**
- **Noise shaping modulators are more robust and easier to implement than predictive modulators**

Sigma-Delta (Delta-Sigma) Modulation

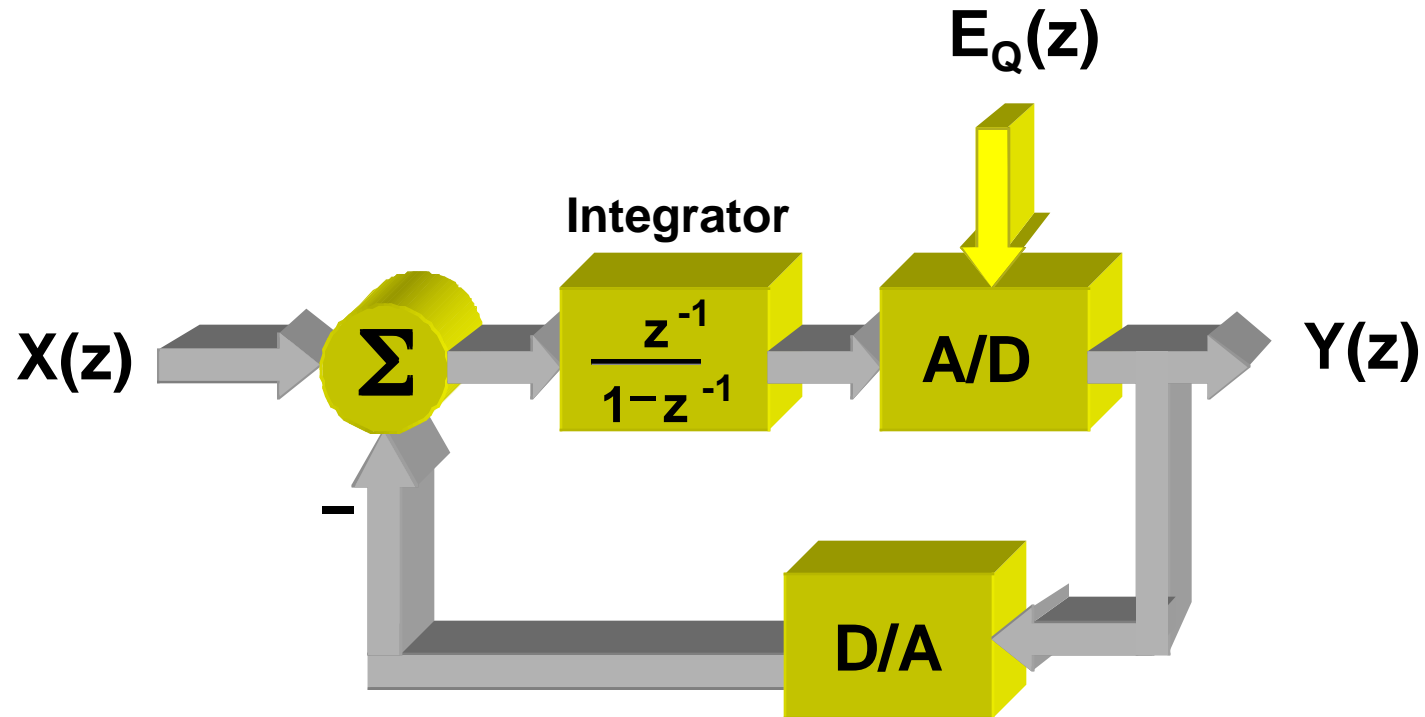


$$Y(z) = z^{-1}X(z) + (1 - z^{-1})E_Q(z)$$

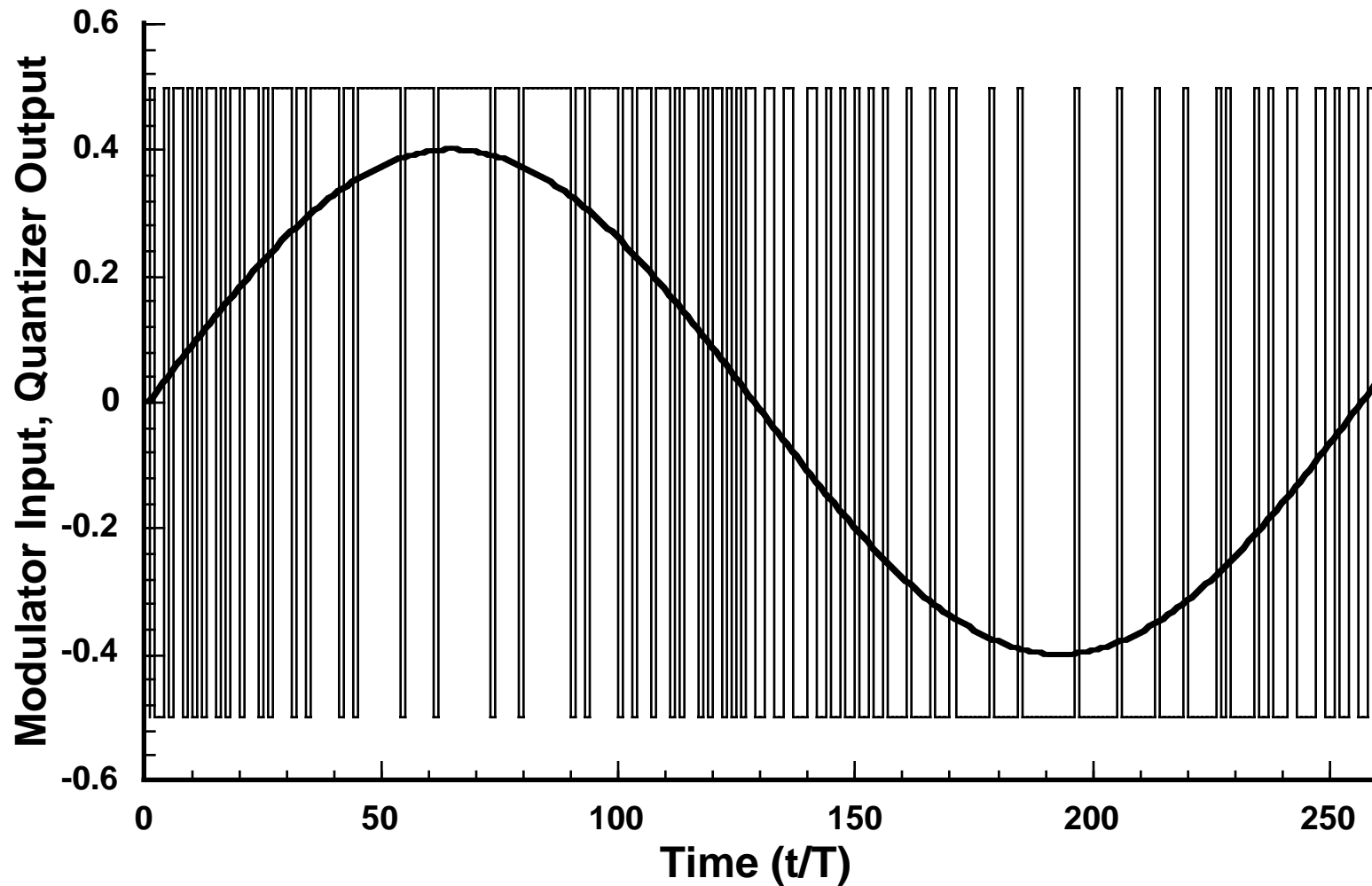$\Sigma\Delta$ Modulator Response (w/ 1-bit Quantization)




Noise Shaping

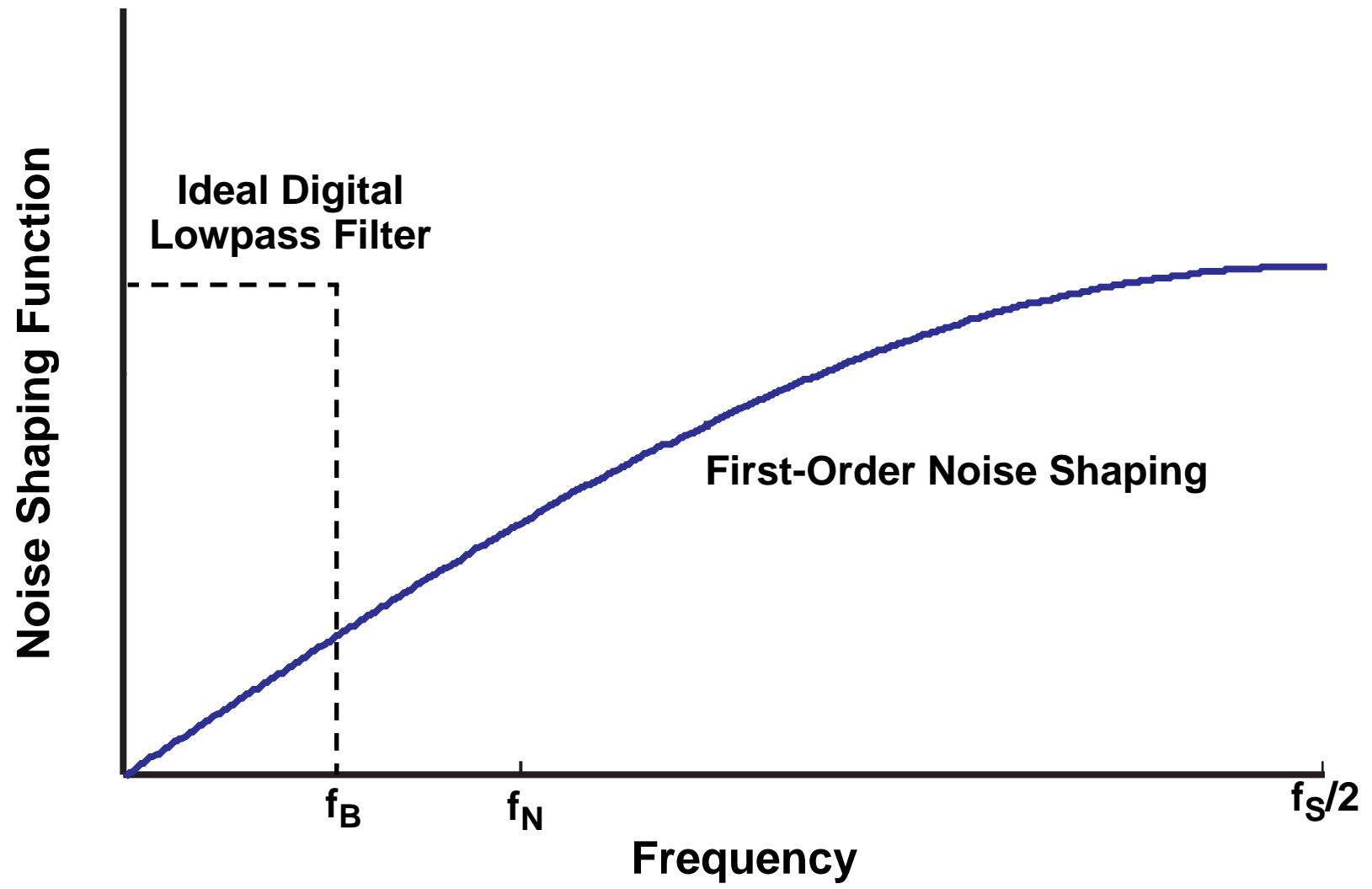


Noise Differencing Modulators (of order L)
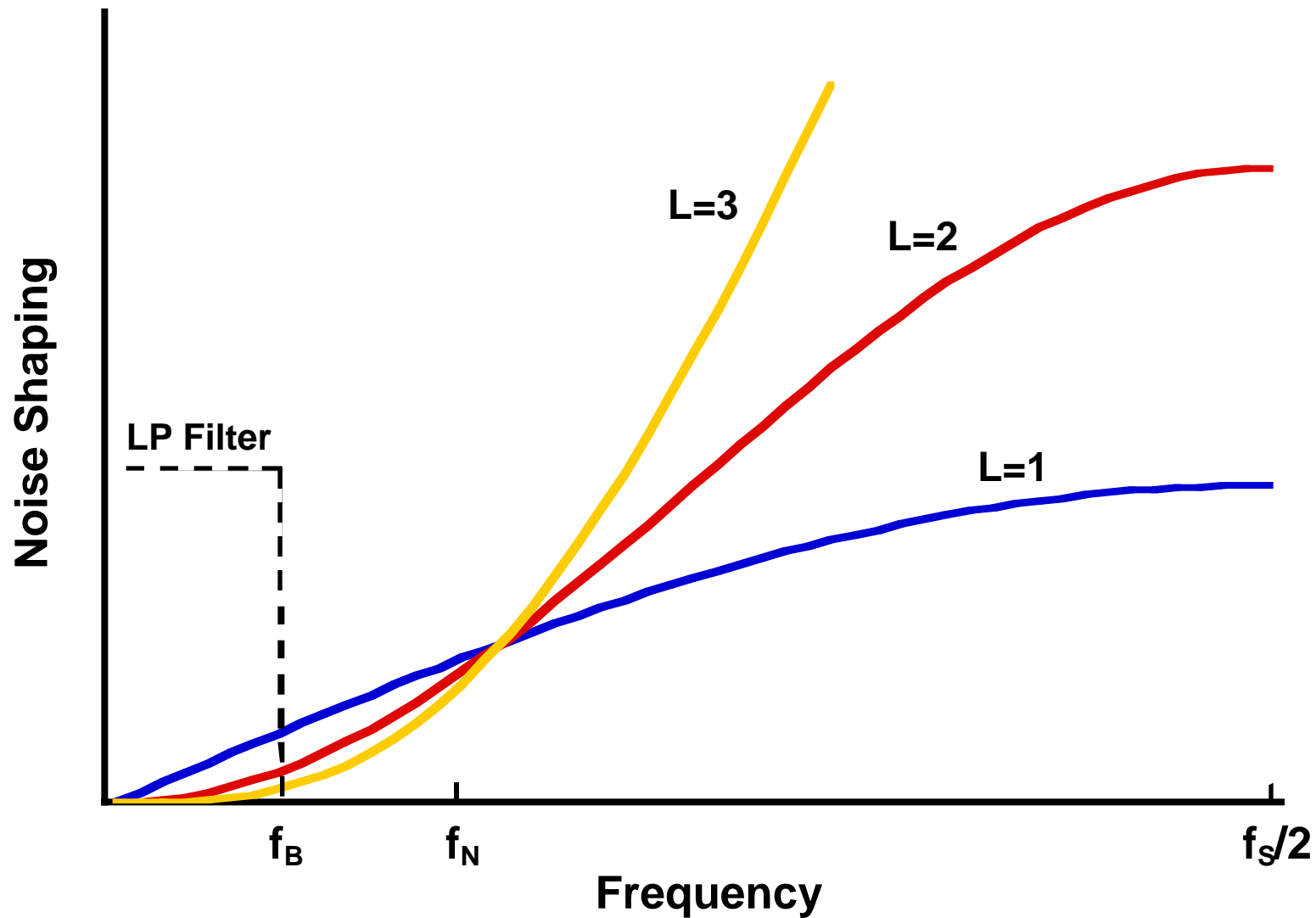
$$Y(z) = z^{-1}X(z) + (1 - z^{-1})^L E_Q(z)$$



Sigma-Delta Modulator Dynamic Range

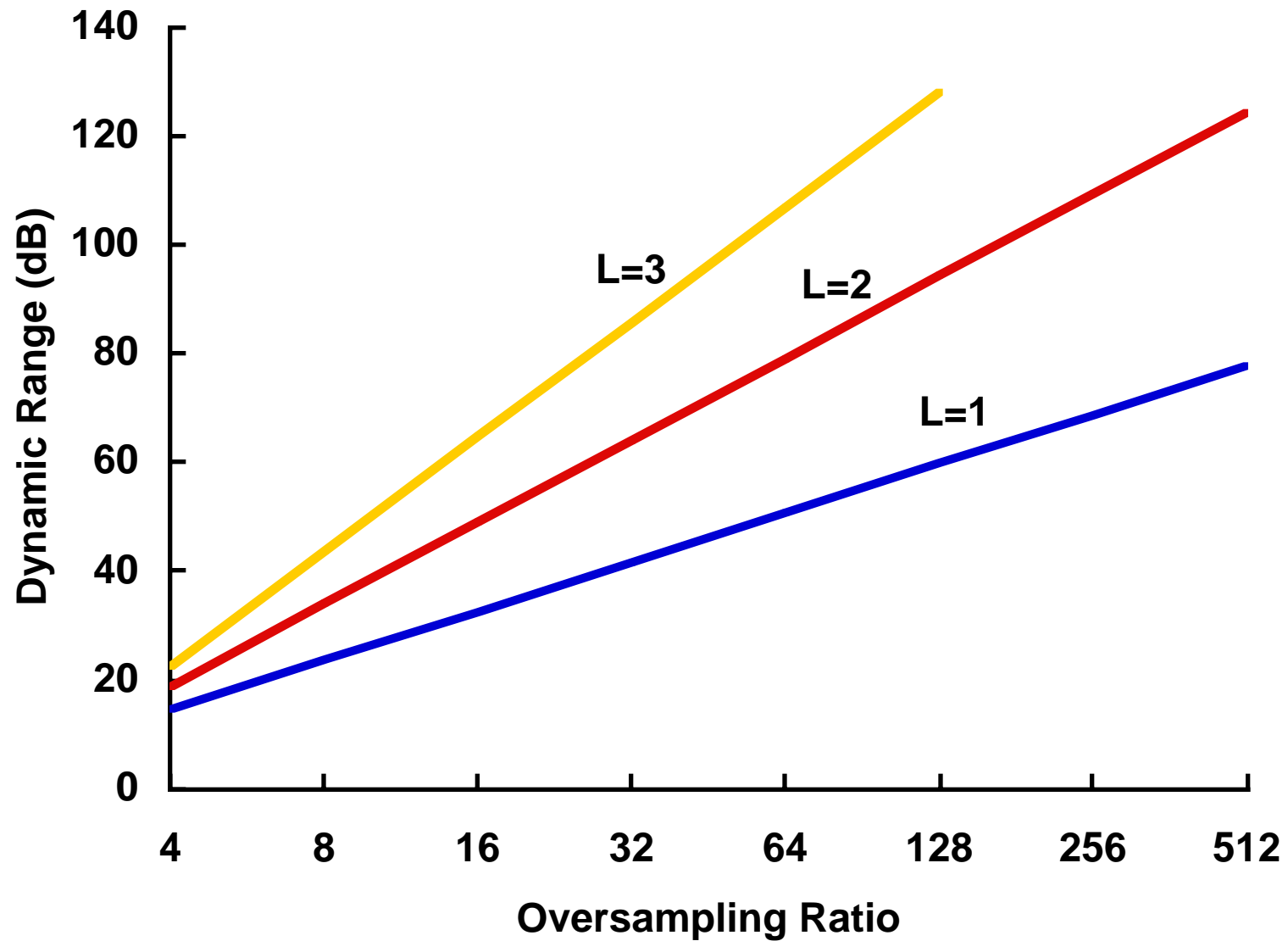

Higher-Order Noise Shaping Modulators


The order of the noise shaping can be increased using either

- **Single quantizer modulators**
 - **Multi-loop noise differencing**
 - **Single-loop with multi-order filter**

or

- **Cascaded (multistage) modulators**

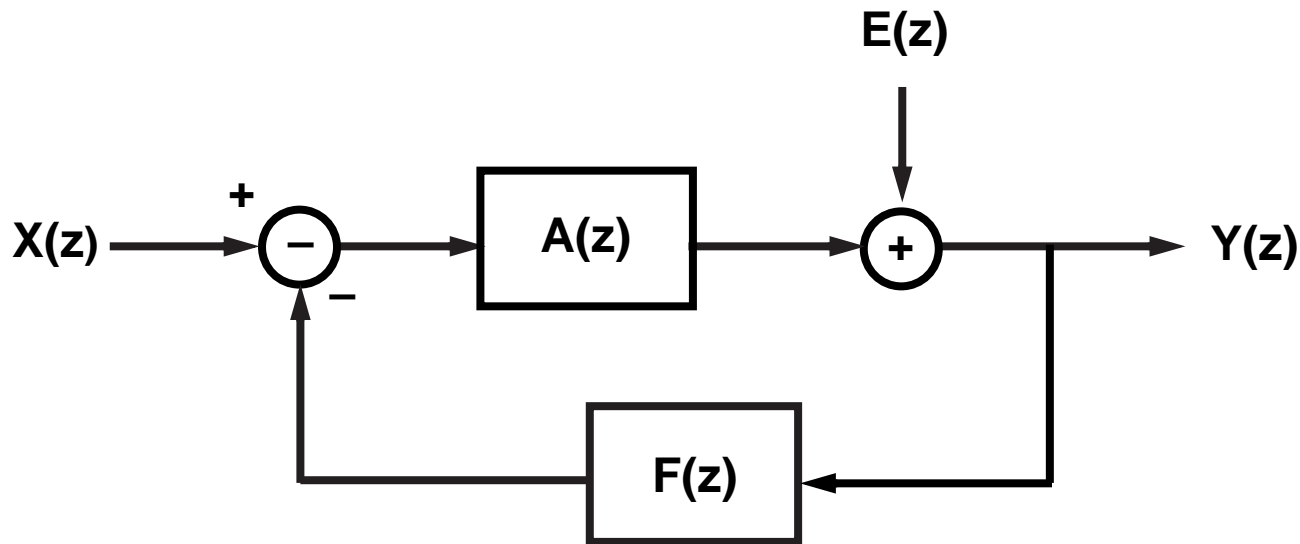Single-Quantizer $\Sigma\Delta$ Modulation



$$Y(z) = H_X(z)X(z) + H_E(z)E(z)$$

where

$$H_X(z) = \frac{A(z)}{1 + A(z)F(z)}, \quad H_E(z) = \frac{1}{1 + A(z)F(z)}$$

and

$$A(z) = \frac{H_X(z)}{H_E(z)}, \quad F(z) = \frac{1 - H_E(z)}{H_X(z)}$$

Noise Differencing Modulators

Class of modulators where:

$$H_X(z) = z^{-1} \quad \text{and} \quad H_E(z) = (1 - z^{-1})^L$$


$$L = 1: \quad H_E(z) = (1 - z^{-1}) \quad \Rightarrow \quad A(z) = \frac{z^{-1}}{1 - z^{-1}}$$

$$F(z) = 1$$



$$L = 2: \quad H_E(z) = (1 - z^{-1})^2 \quad \Rightarrow \quad A(z) = \frac{z^{-1}}{(1 - z^{-1})^2}$$

$$F(z) = 2 - z^{-1} \quad (\neq 1)$$

Second-Order Implementation

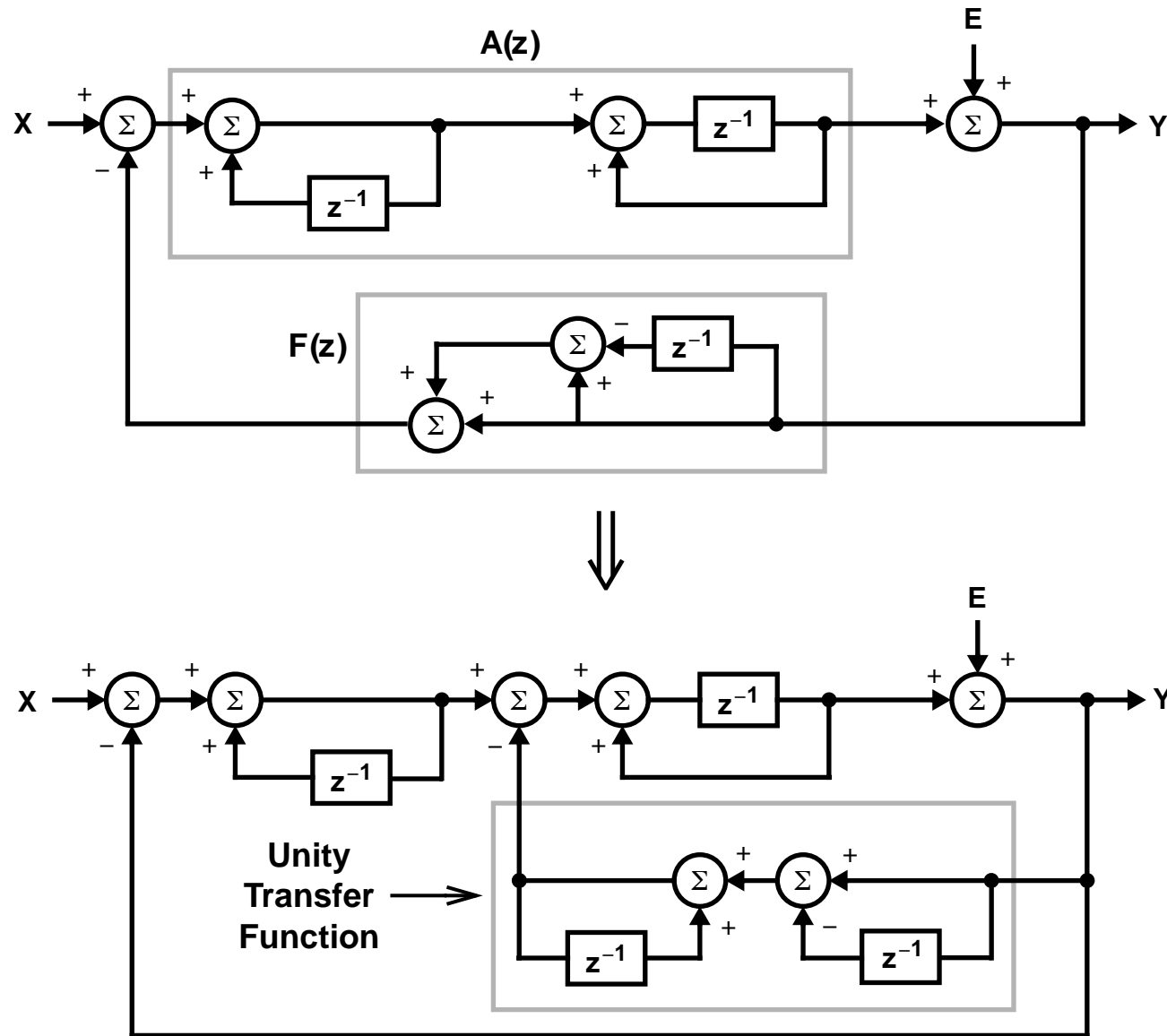


Second-Order $\Sigma\Delta$ Modulator

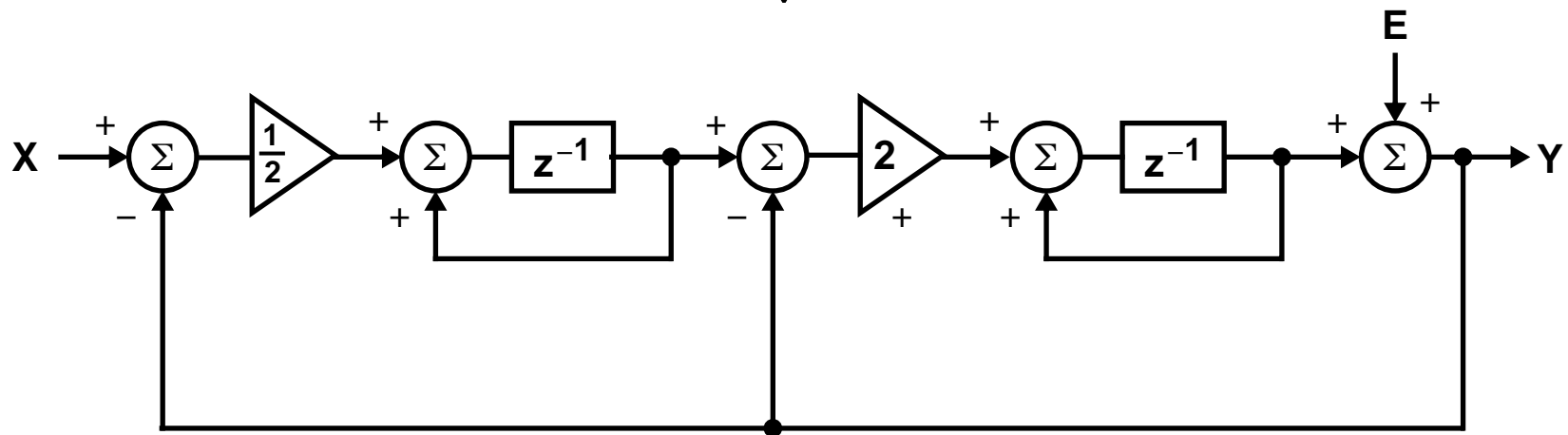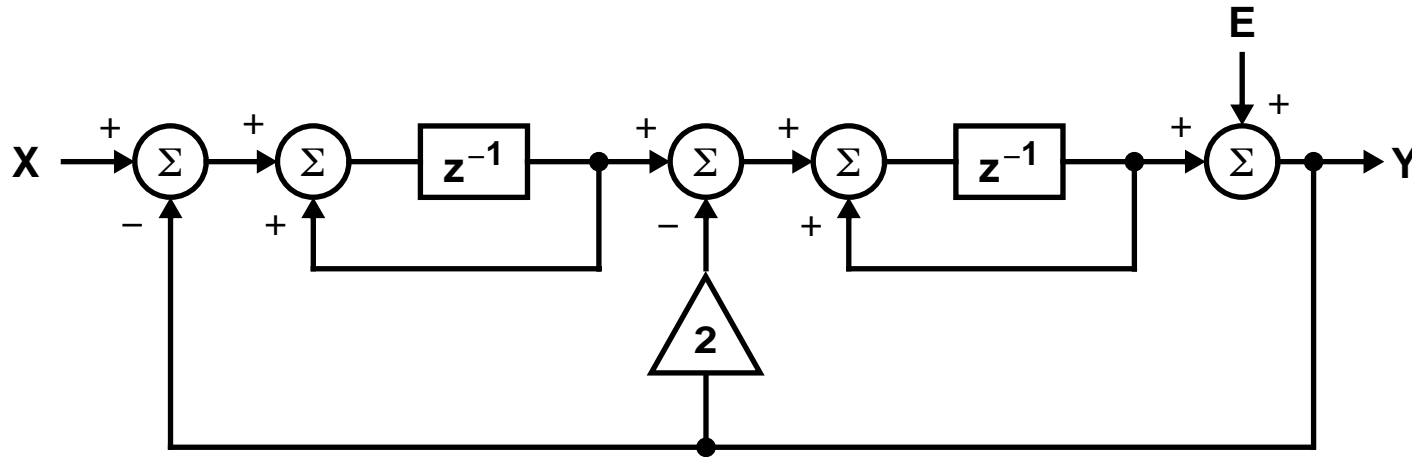

Second-Order Noise Differencing $\Sigma\Delta$ Modulator

(with 1-bit quantization)

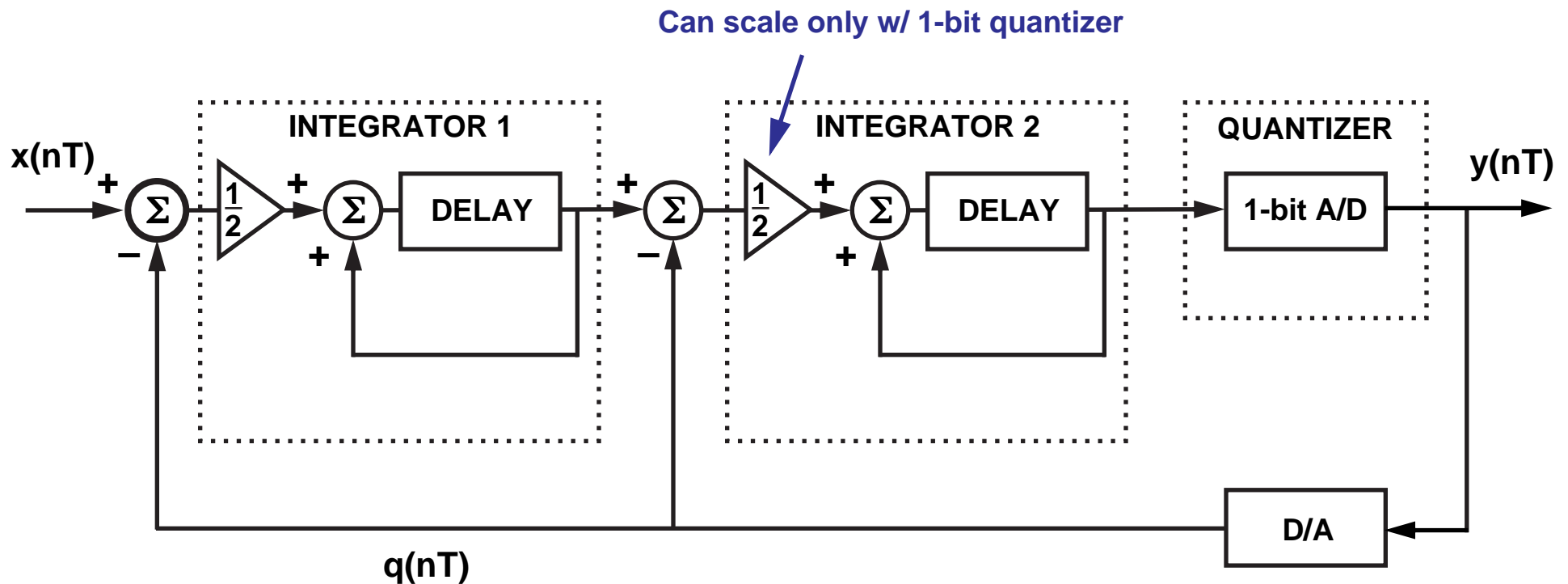


- Key building block for cascaded modulators

Cascaded $\Sigma\Delta$ Modulators


- **Quantizer error quantized by subsequent stage and then filtered and subtracted digitally**
- **Cancellation of lower-order noise shaping terms depends on matching of analog and digital paths**
- **No potential instability**

Cascaded Oversampling ADC

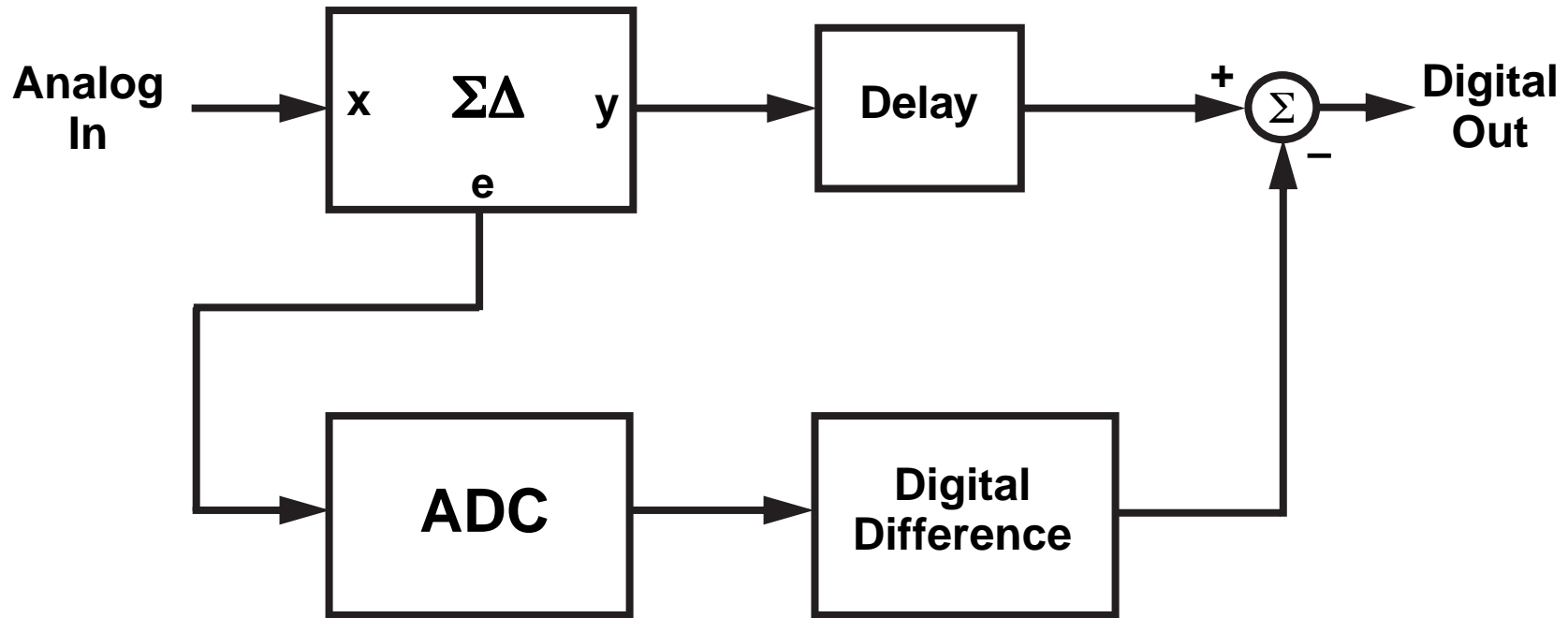


Matches noise shaping of quantization error in first stage

Maximum Dynamic Range Improvement

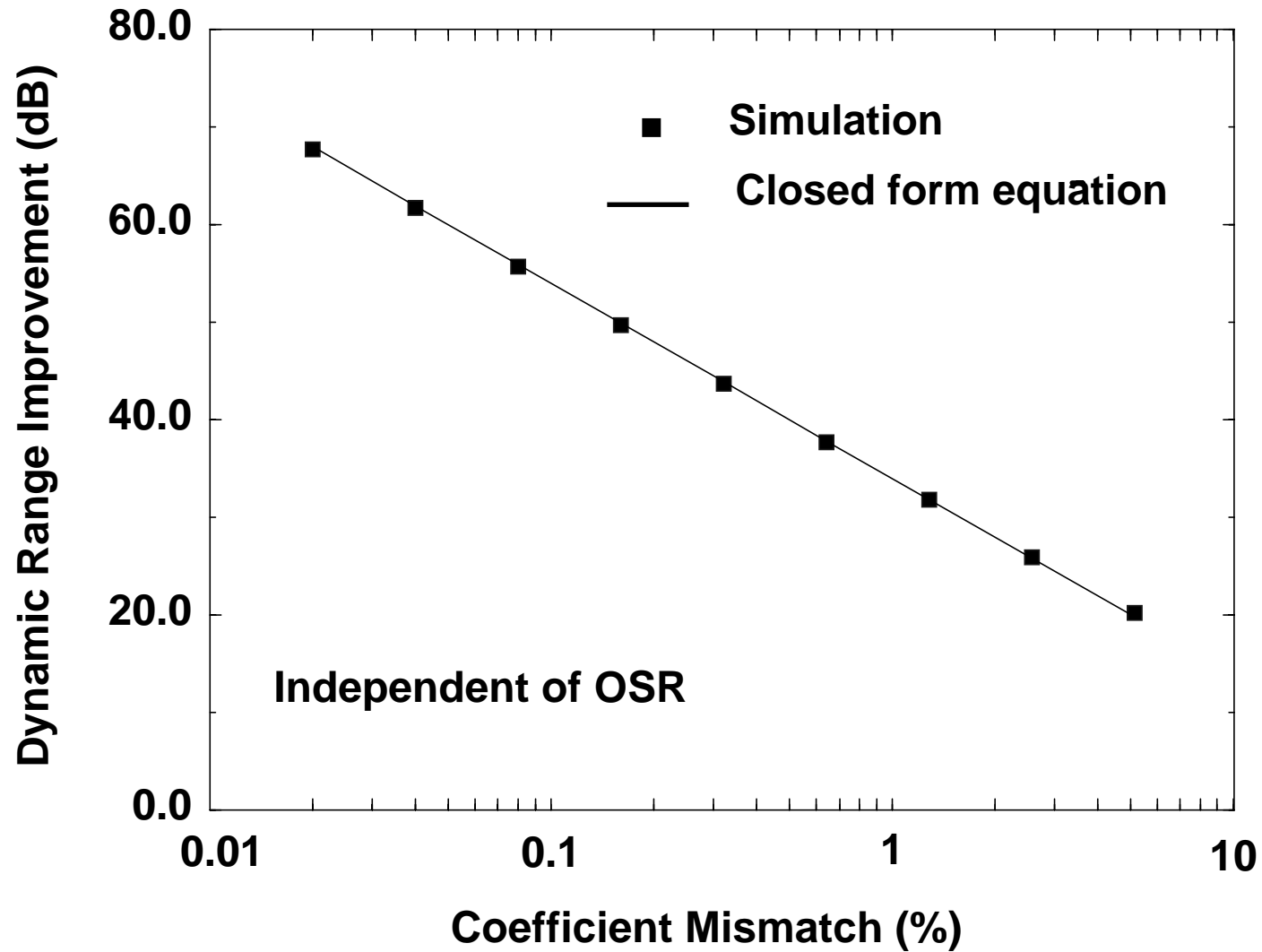

Third-Order (2-1) Cascaded Modulator

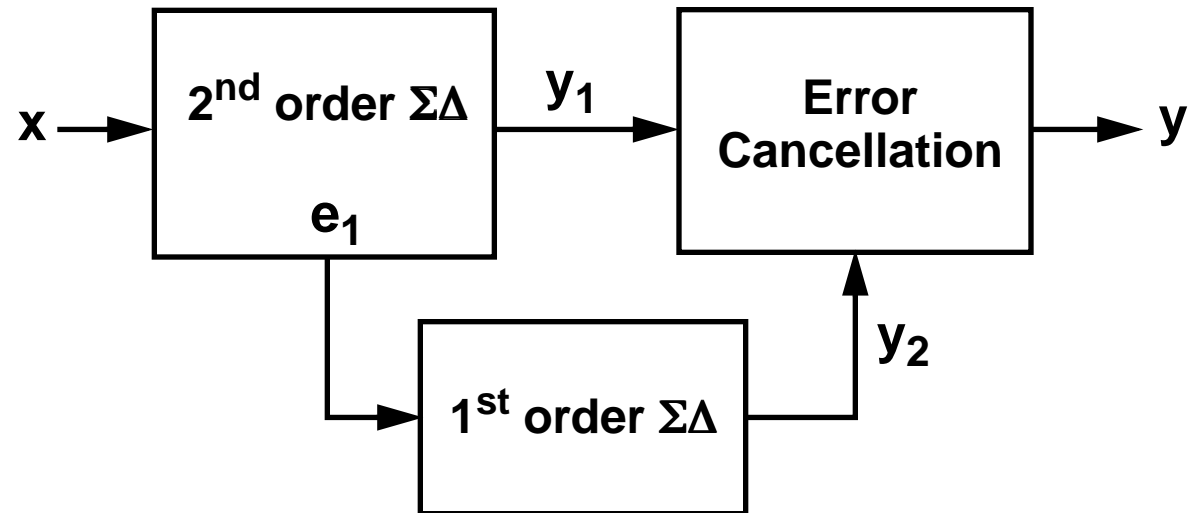


$$Y_1 = z^{-2}X + (1 - z^{-1})^2 E_1$$


$$Y_2 = z^{-1}E_1 + (1 - z^{-1}) E_2$$

$$Y = z^{-1}Y_1 - (1 - z^{-1})^2 Y_2 = z^{-3}X - (1 - z^{-1})^3 E_2$$

Matching Error in 2-1 Cascade

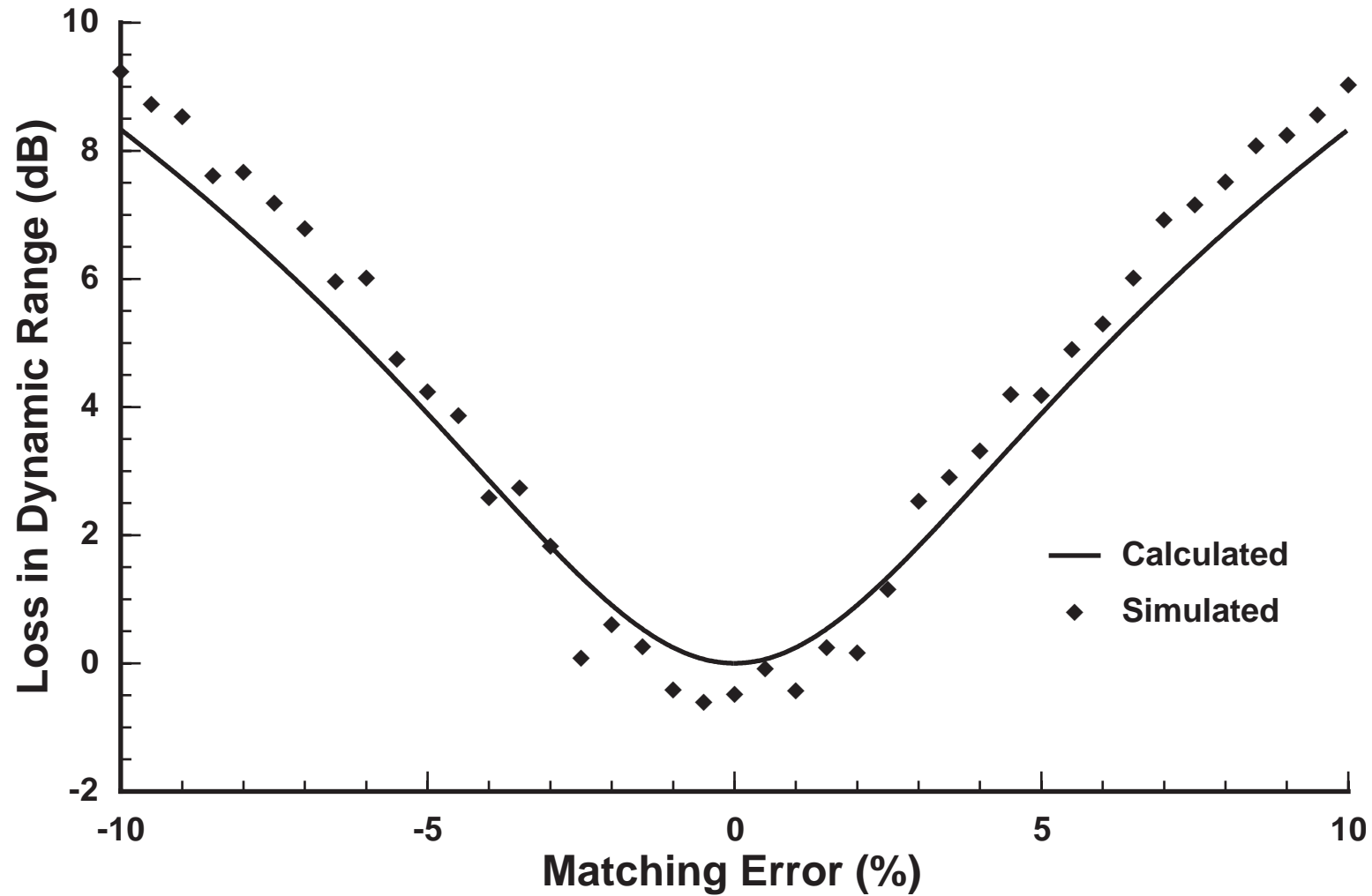

2-1 Spectrum with Mismatch

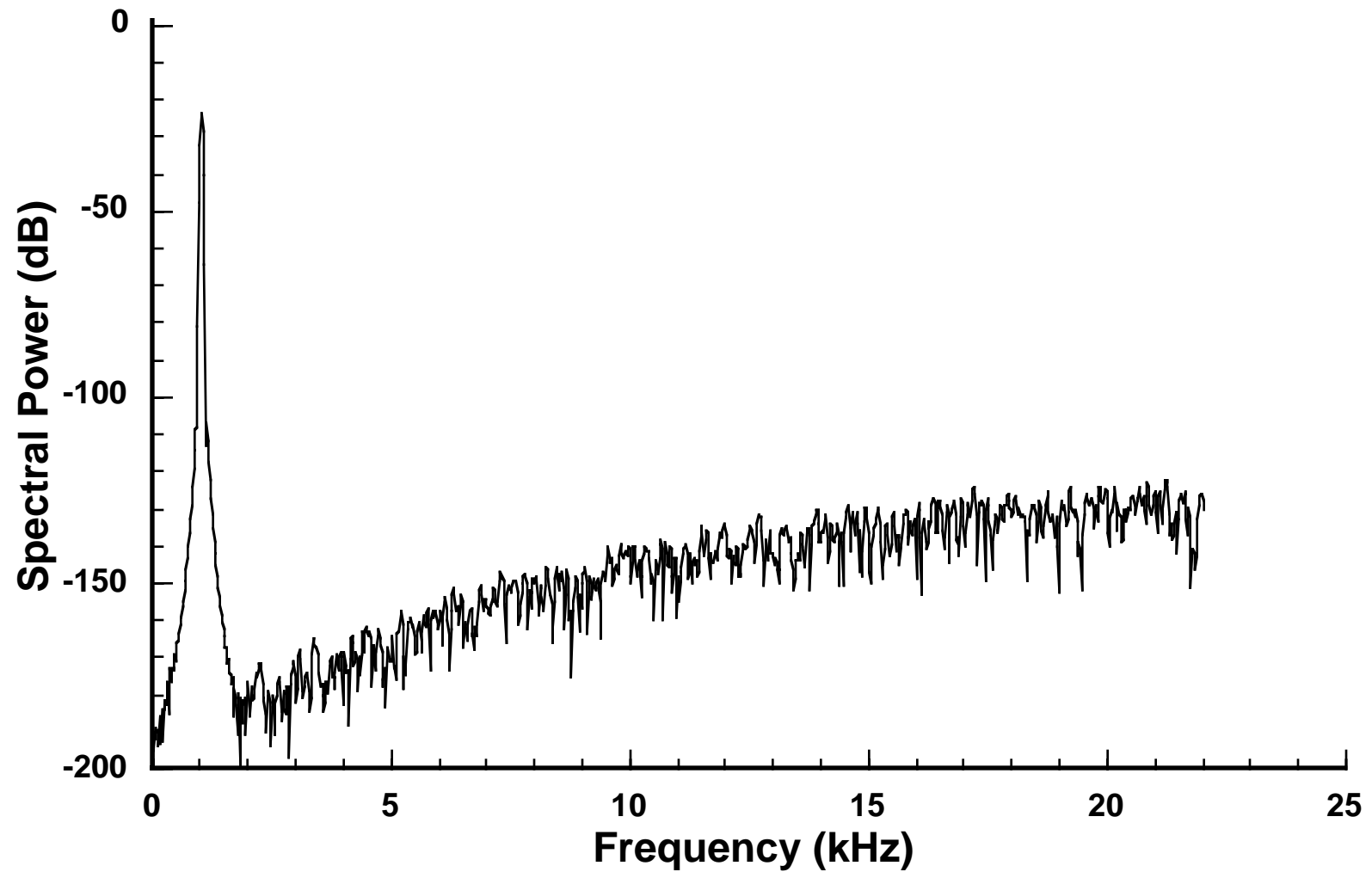


Advantages of 2-1 Cascade

- **Low sensitivity to precision of analog path**
- **Suppression of spurious noise tones resulting from correlation of quantization noise with input**
- **Considerable design flexibility**
- **No potential instability**



Digitizing MHz-Bandwidth Signals

- **Oversampling modulators dominate precision A/D conversion at modest signal bandwidths**
 - e.g. digital audio
 - exploit large oversampling ratios
- **Challenge is to digitize signals where the oversampling ratio is constrained by technology (MHz bandwidths)**
- **Possible approaches based on cascade architectures include**
 - multibit quantization in second stage
 - merged quantization
 - distributed noise shaping zeros
 - multilevel quantization with digital linearization

Lowpass Cascade Architecture

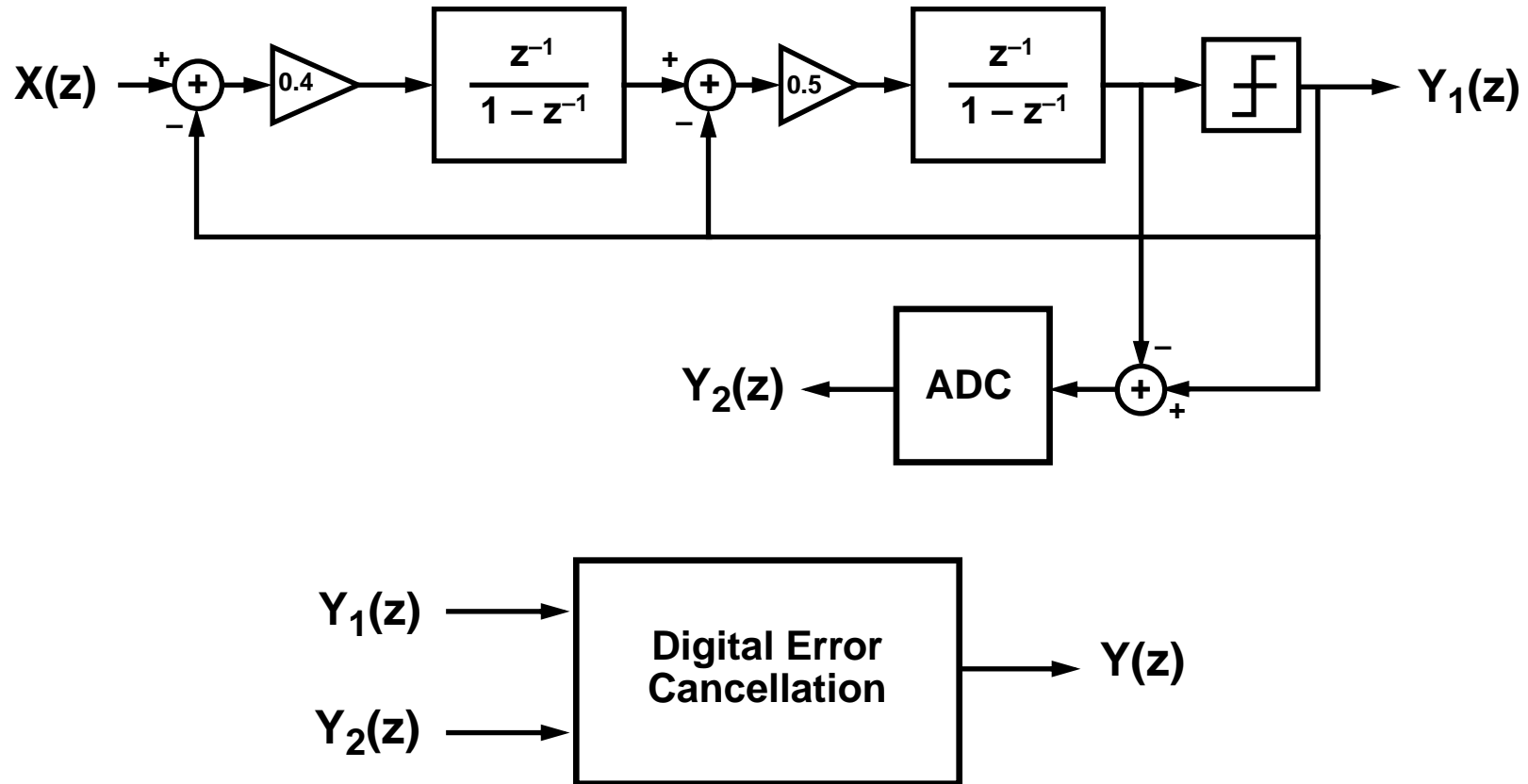


Embedded Quantization *

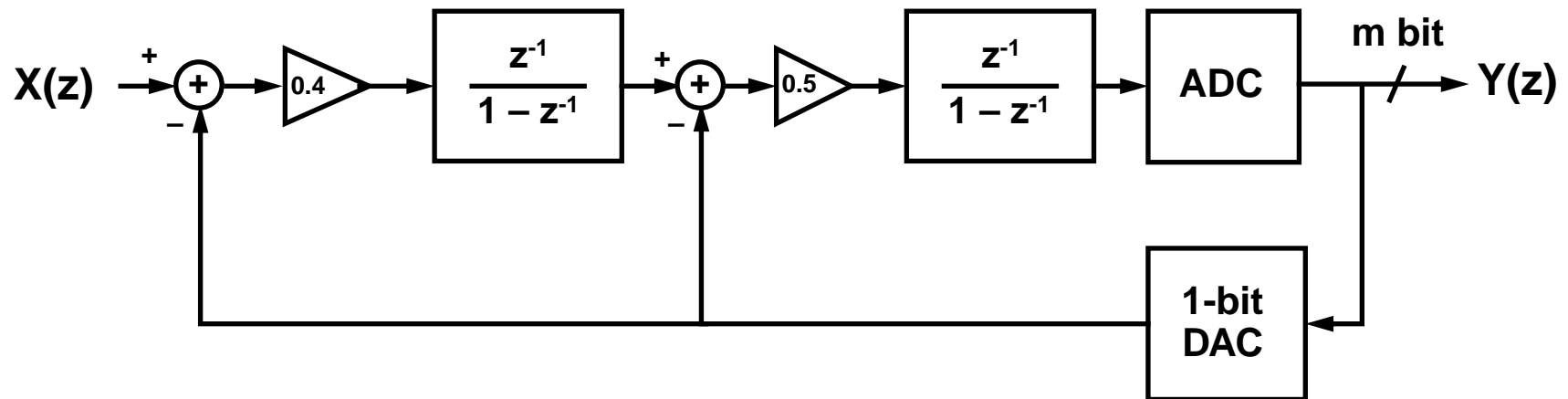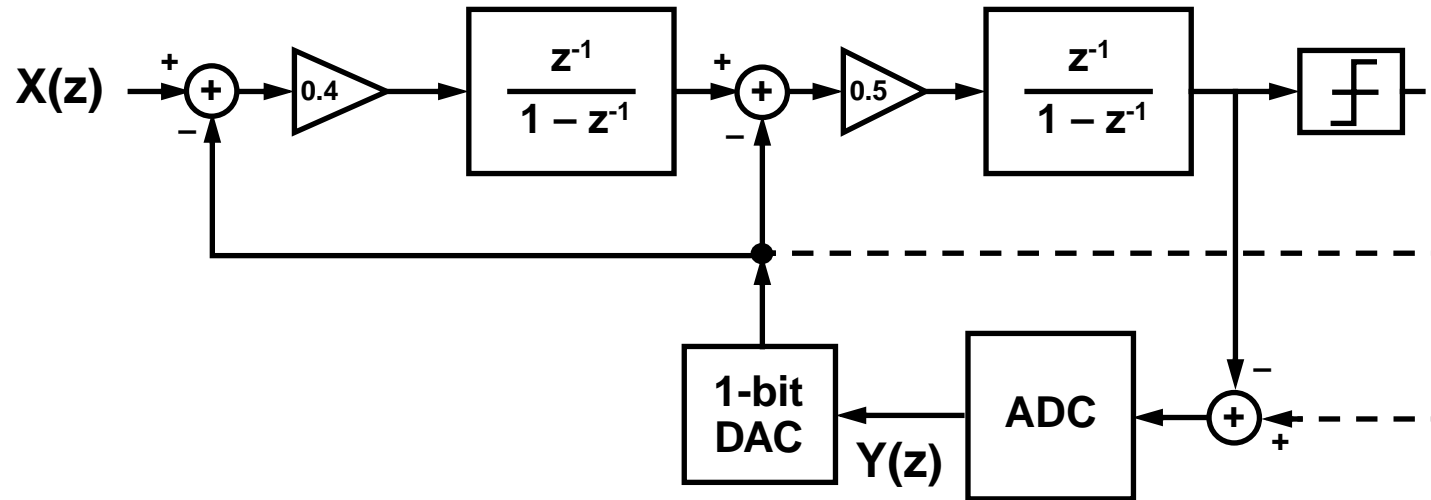


* A. Tabatabaei, 99 VLSI Ckt Symp


Model of Merged Quantizer Modulator

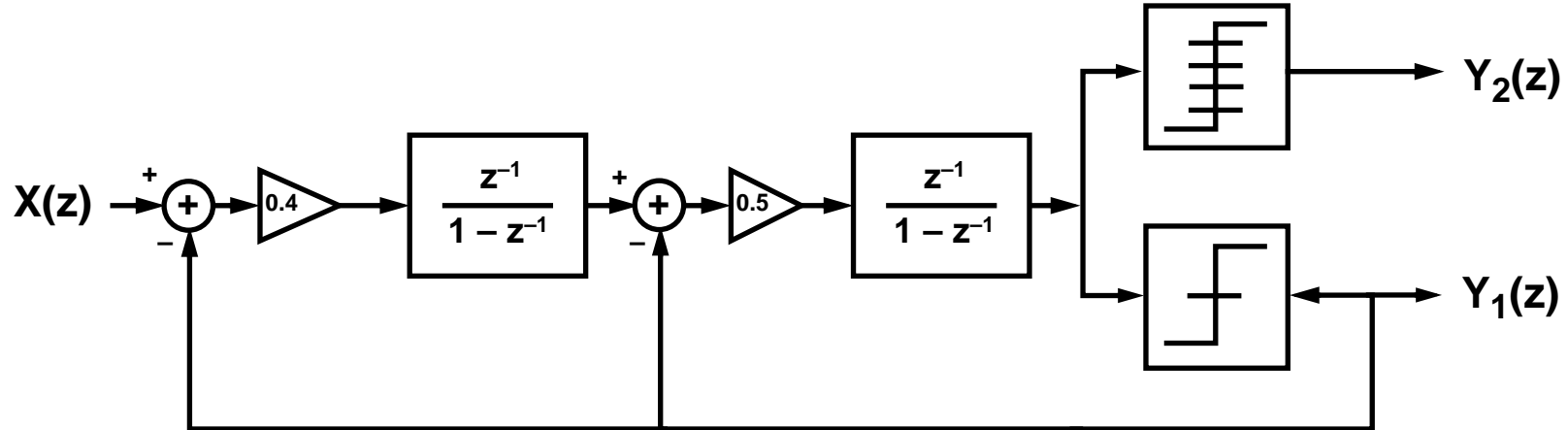


Implementation of Embedded ADC

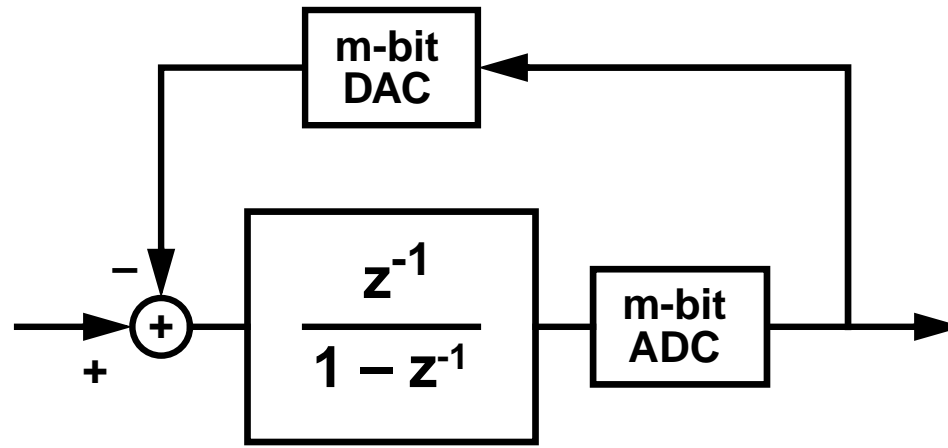

Noise Shaped Error

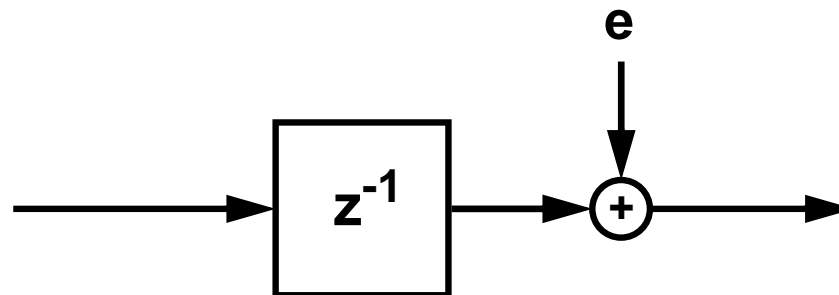


Lowpass Modulator with Embedded ADC *

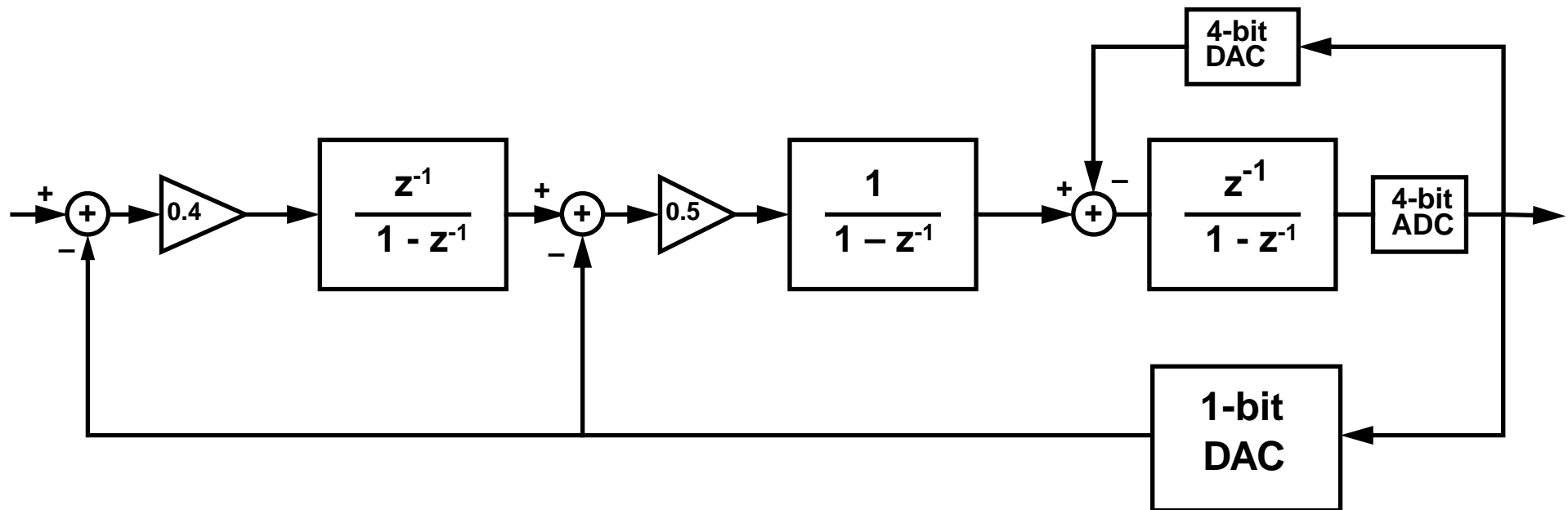


- Delay unaltered
- Stability maintained by 4-bit quantization

2-2 Cascaded Modulator

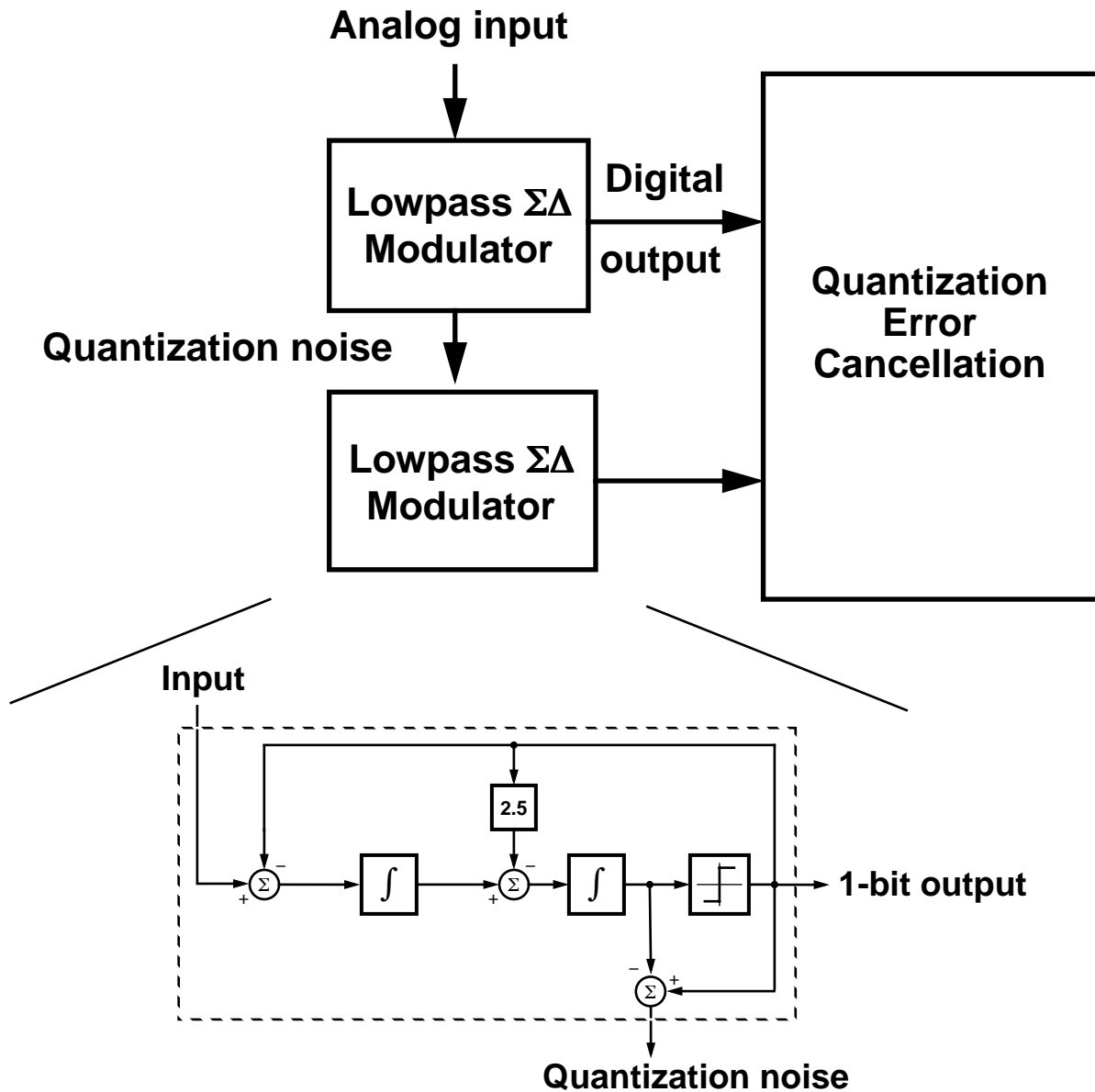

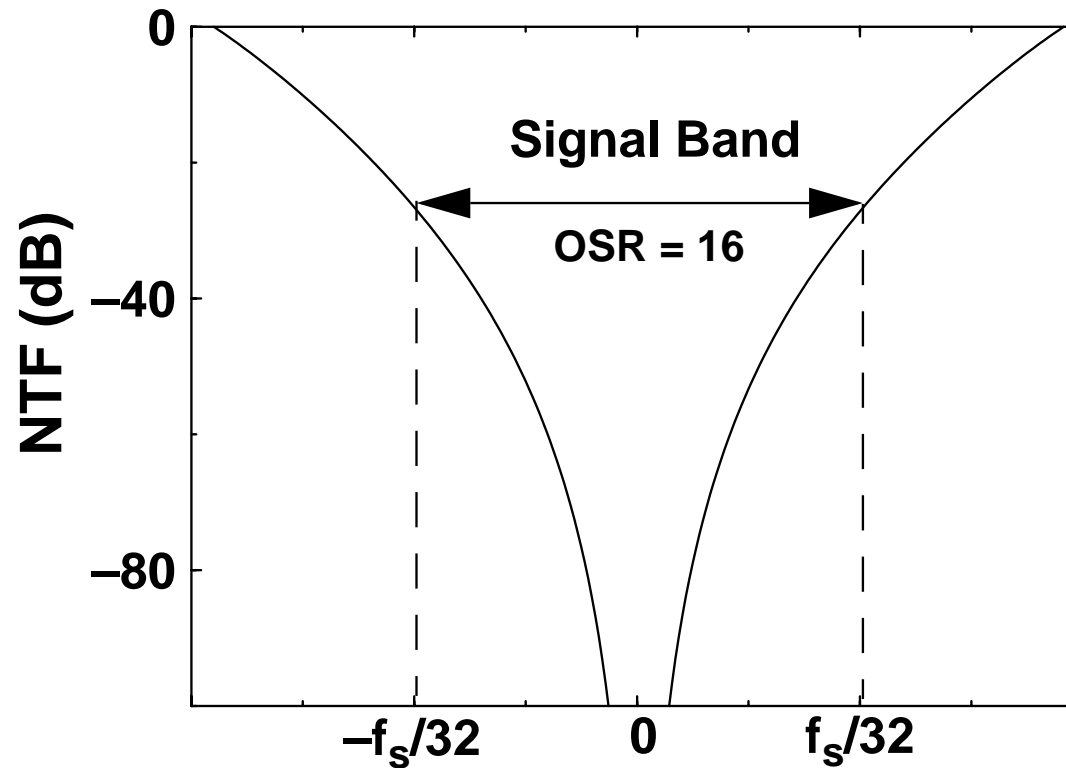
Noise Transfer Function for 2-2 Lowpass Cascade



NTF for a two-stage lowpass cascade (2-2):

- $NTF = N_1 \times N_2 = (N_{LP})^2$
- $|NTF| > 0$ dB for $OSR < 8$


Distribute Zeros Across the Signal Band

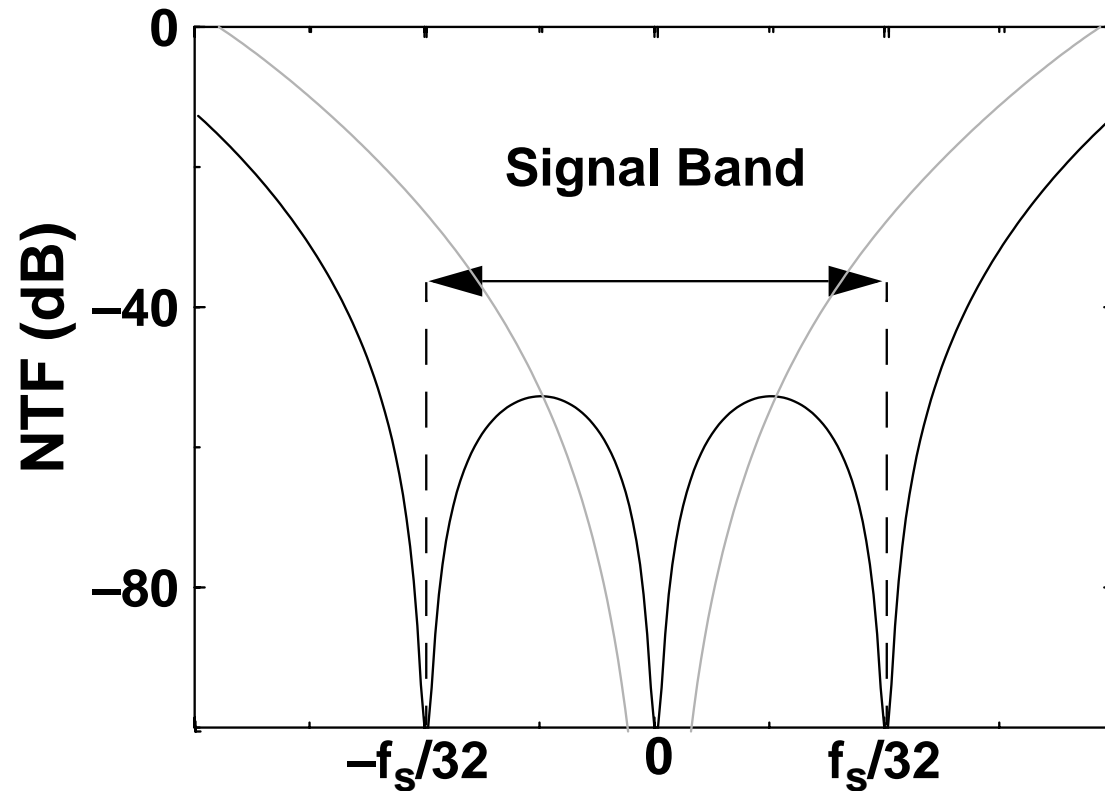

Cascade lowpass and bandpass stages:



- Reduces inband noise
- $NTF = N_1 \times N_2 = N_{LP} \times N_{BP}$

Lowpass-Bandpass Cascaded Modulator *

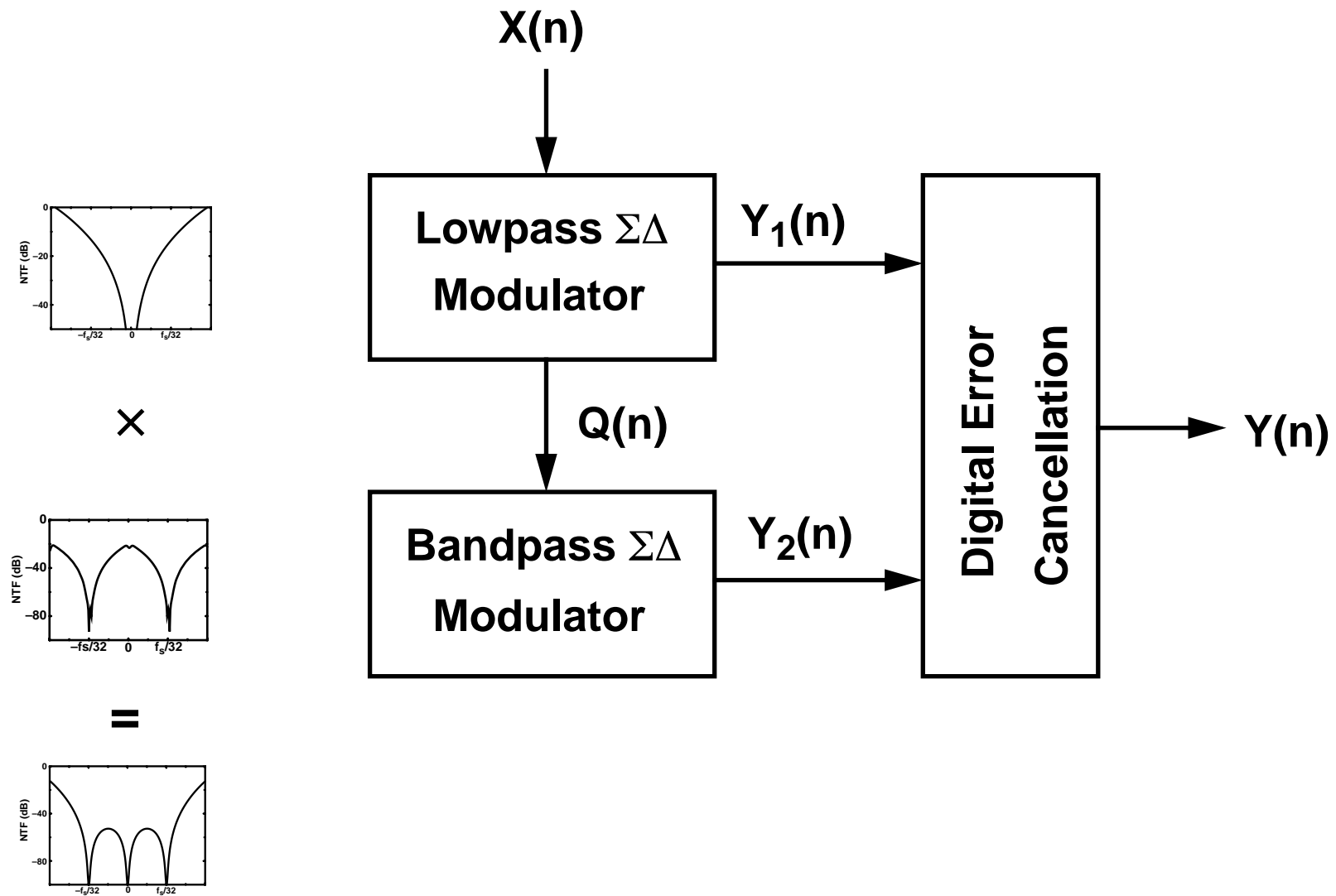


* A. Tabatabaei, JSSC 12/00


Bandpass Second Stage

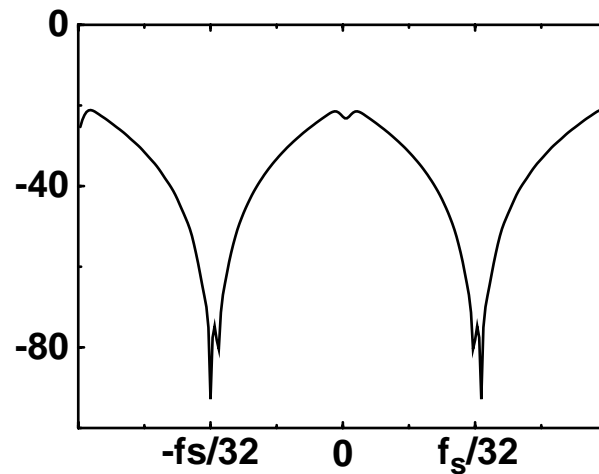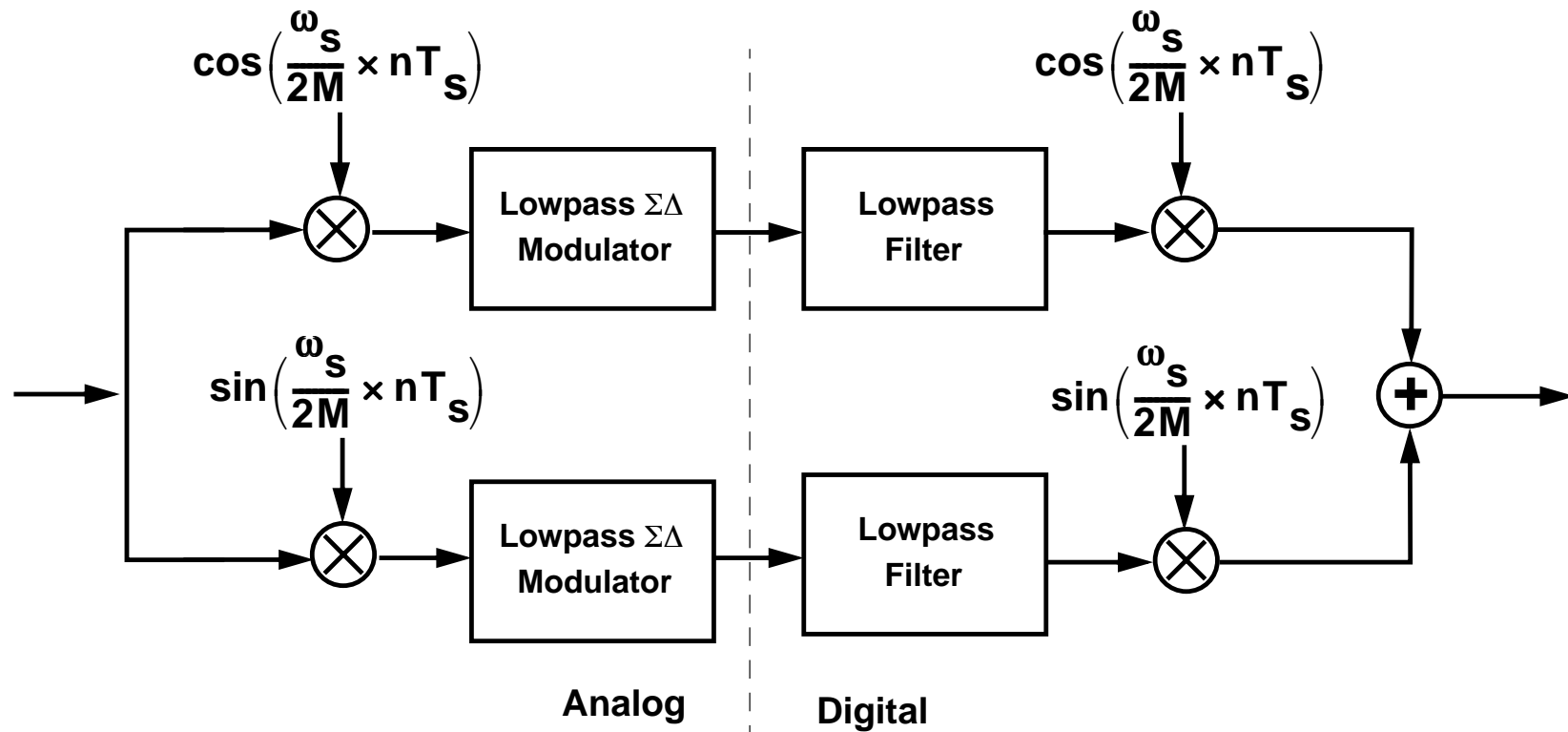


2-2-2/2 Lowpass Modulator

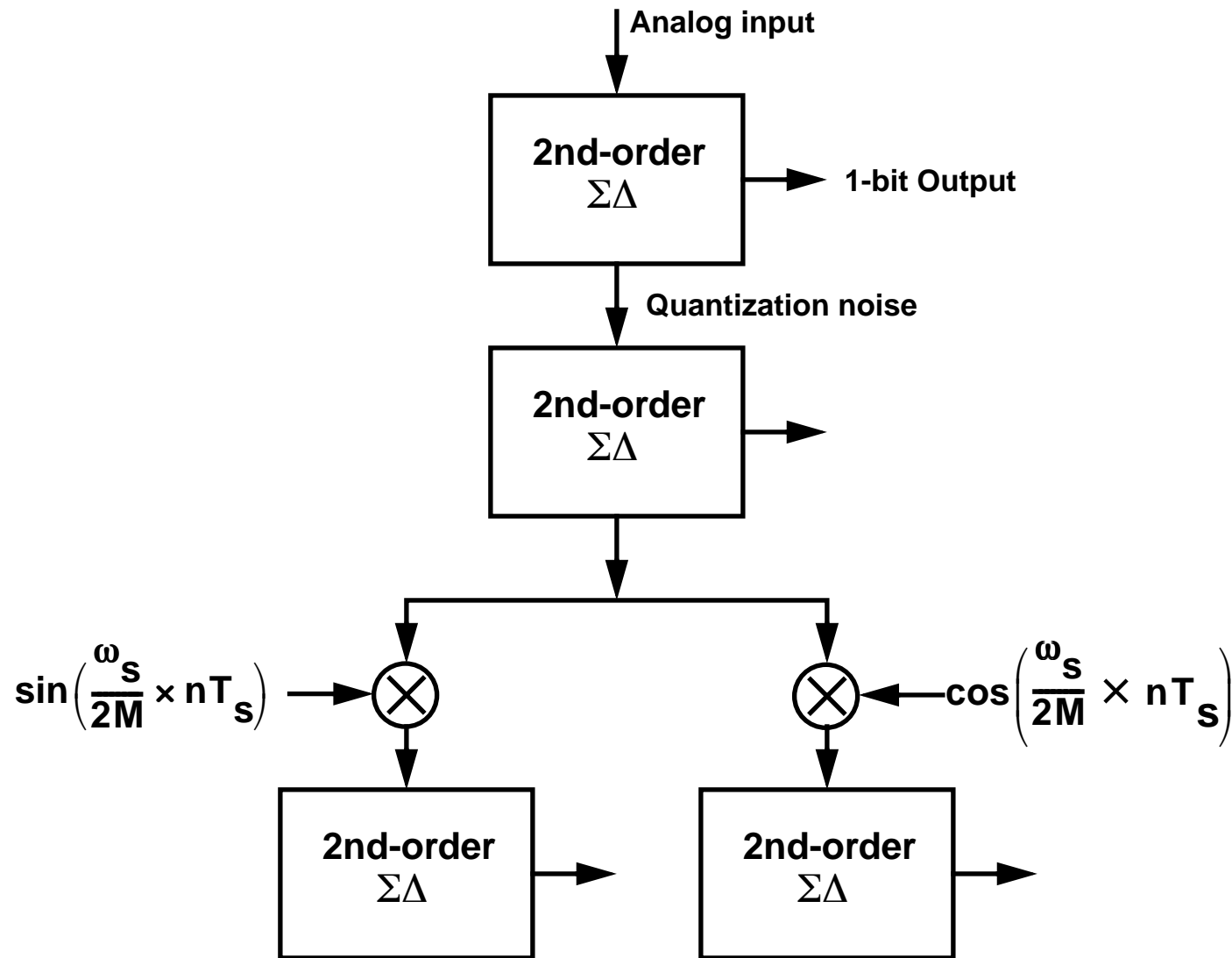


Bandpass Stage Mixer

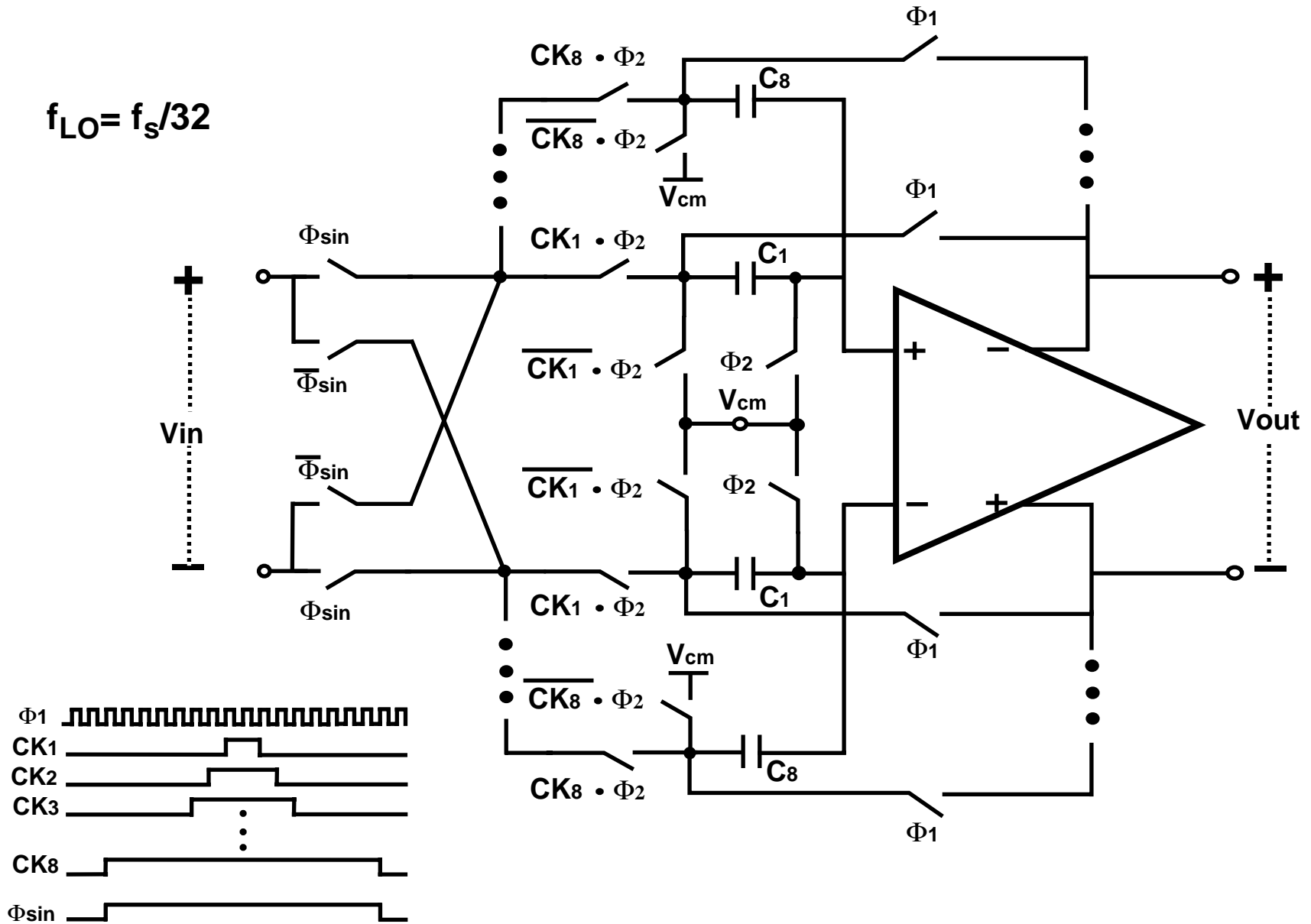


$f_s/4$ Two-Path Bandpass Modulator

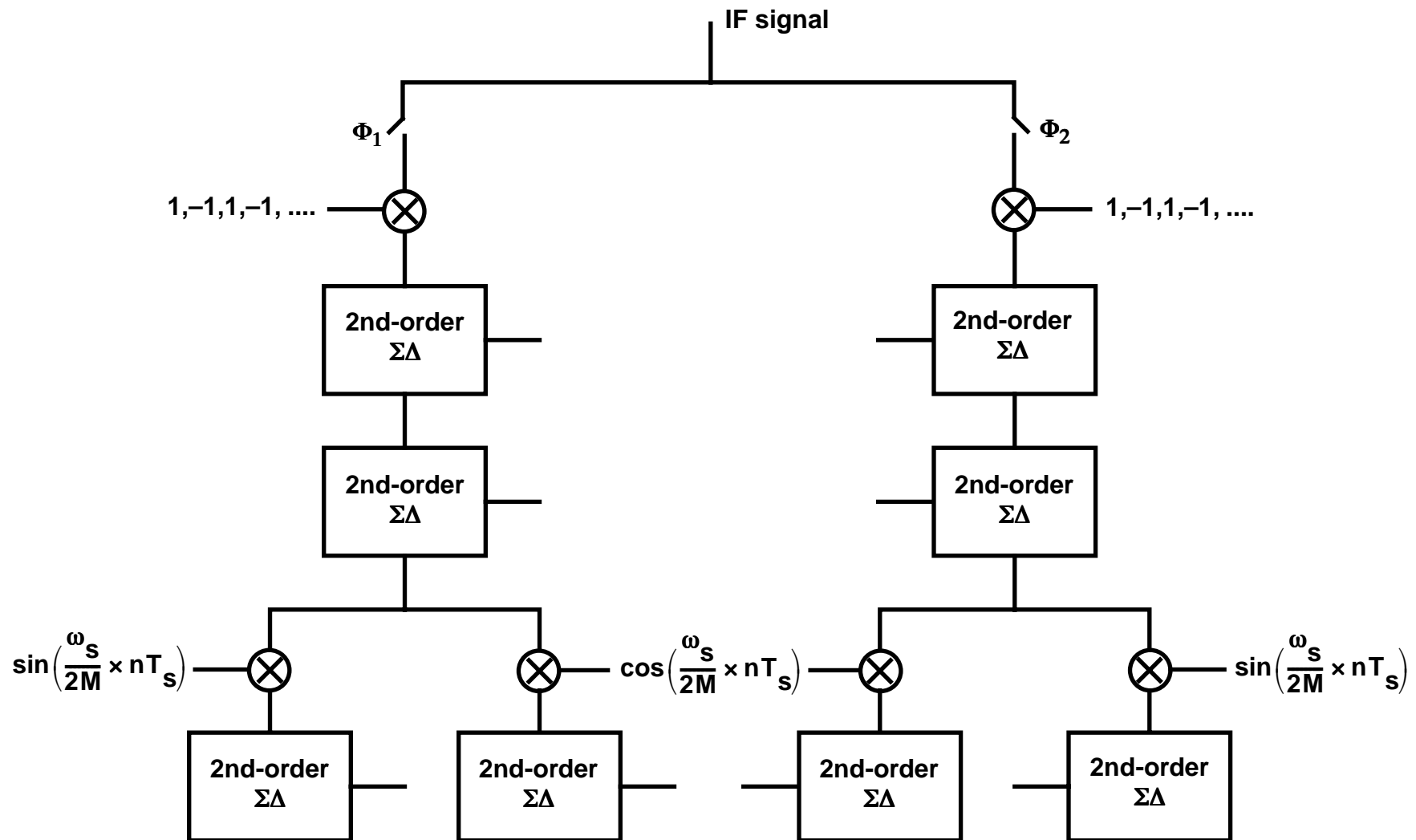


Chip Micrograph

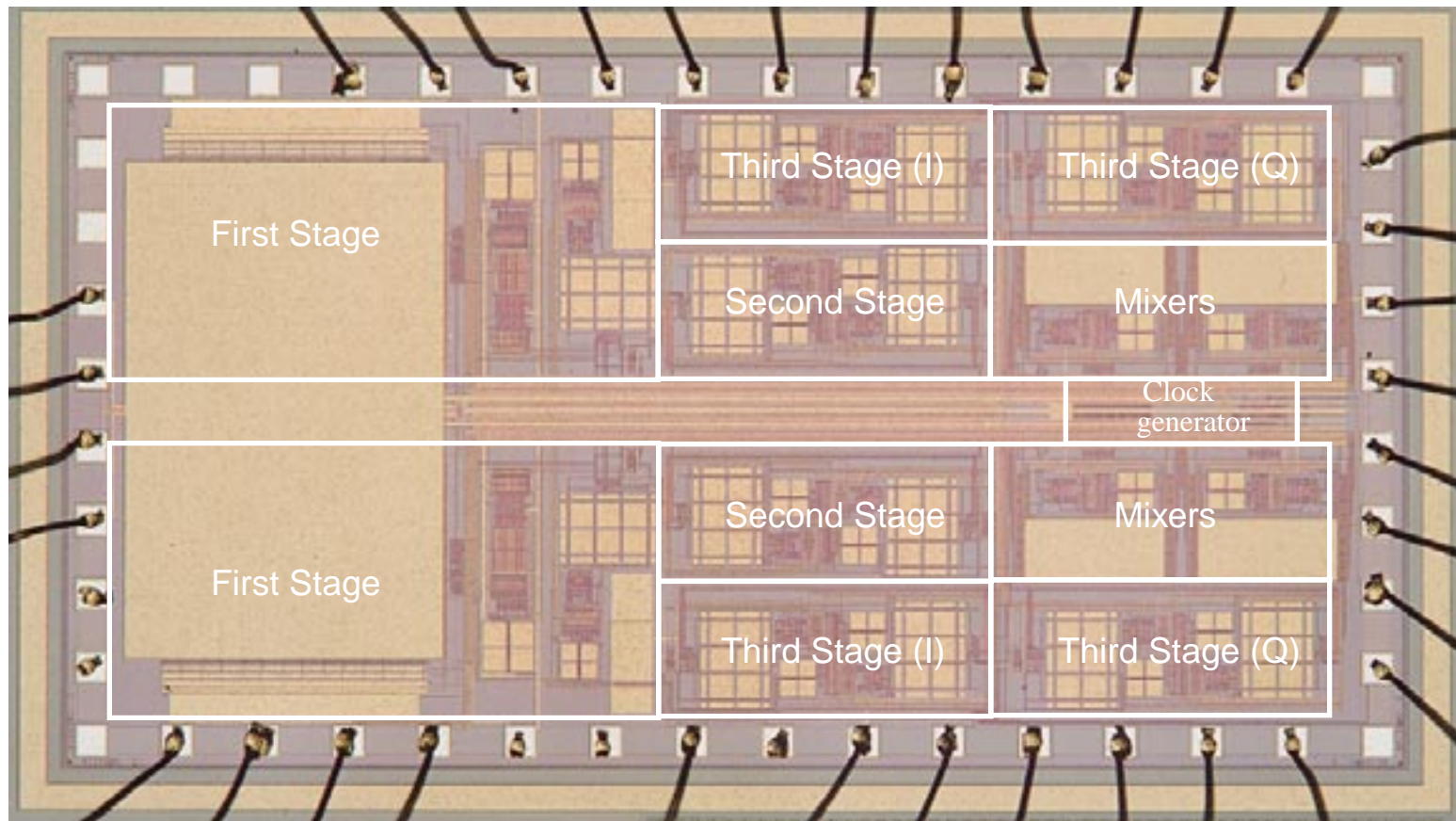

Measured SNR and SNDR

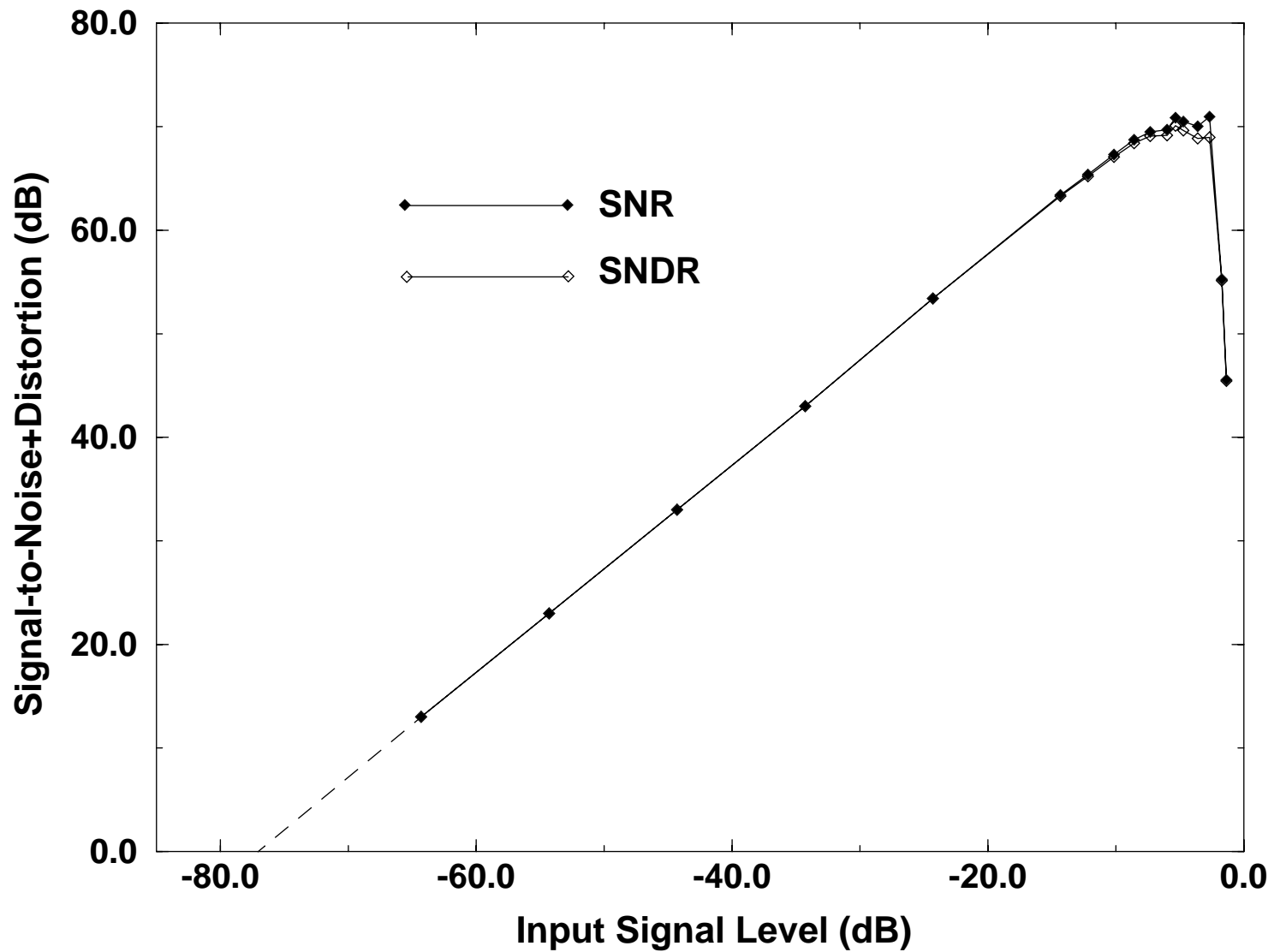

Measured Output Spectrum

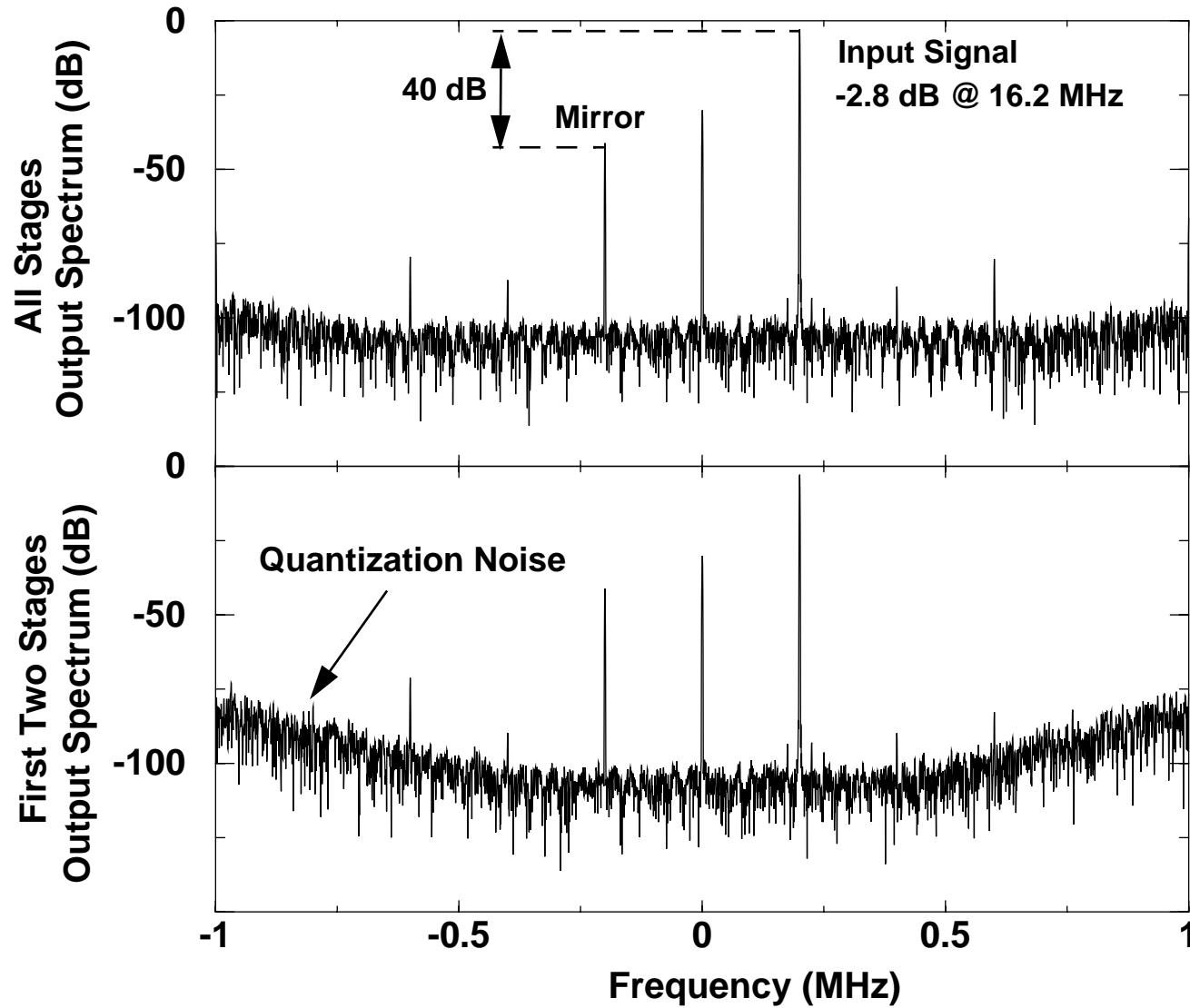

Performance Summary


Sampling rate	64 MS/s
Passband	2 MHz centered at 16 MHz
Oversampling ratio	16
Dynamic range	75 dB
Max SNDR	70 dB
Power supply	2.5 V
Power dissipation	140 mW
Technology	0.24-μm, 5-metal CMOS
Area	2 mm \times 1.7 mm

Bandpass Oversampling D/A Conversion *


- **Consider the use of bandpass oversampling D/A conversion in wireless communications transmitters**
- **Move IF into the digital domain to eliminate**
 - **dc offset**
 - **I & Q mismatch**
- **Merge D/A conversion, noise shaping, reconstruction and IF mixing**
- **Explore the use of cascaded digital noise shaping for D/A conversion**

* D. Barkin, 03 VLSI Ckt Symp

Traditional Transmitter Architecture

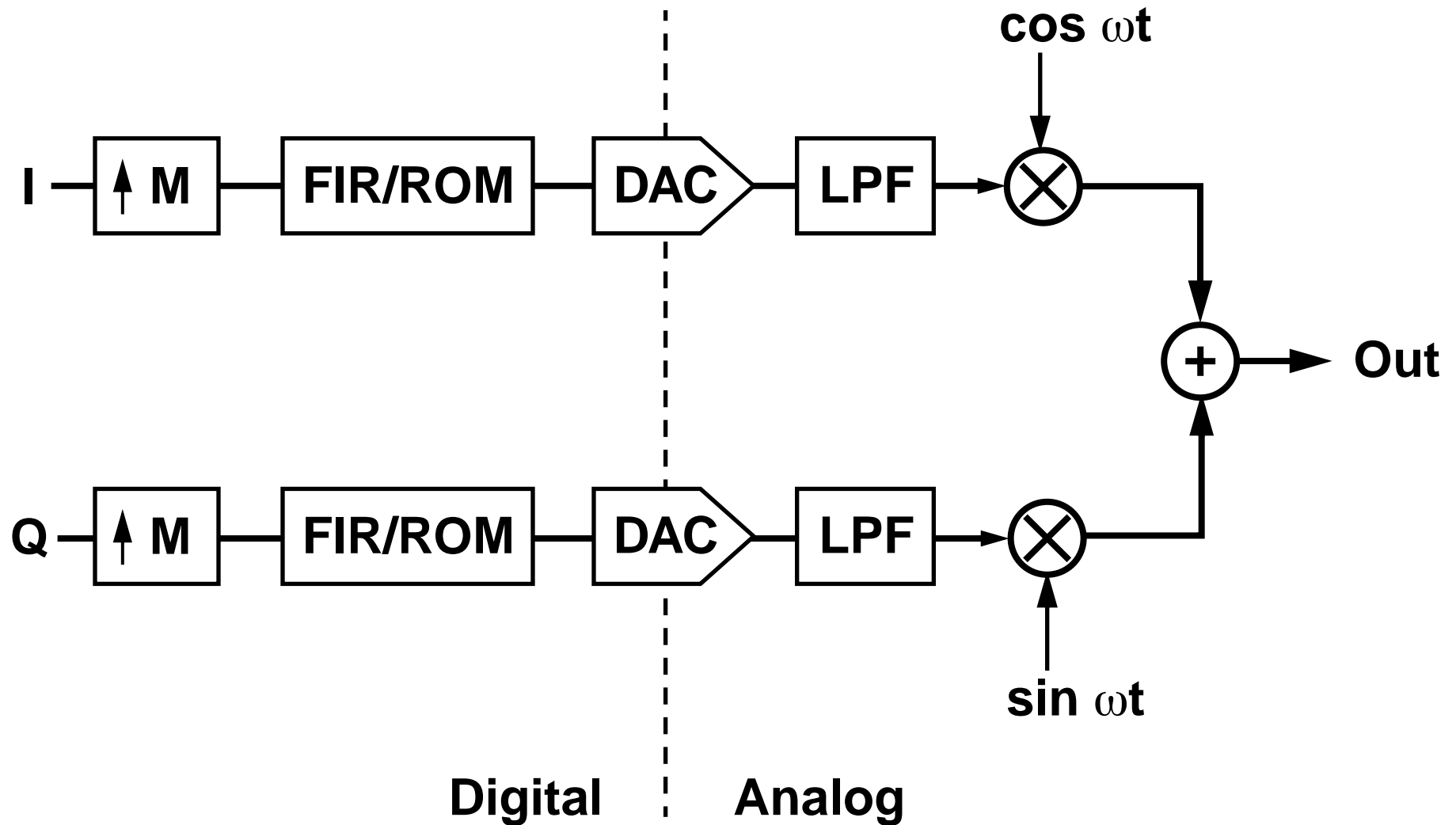


Cascaded Bandpass Oversampling DAC

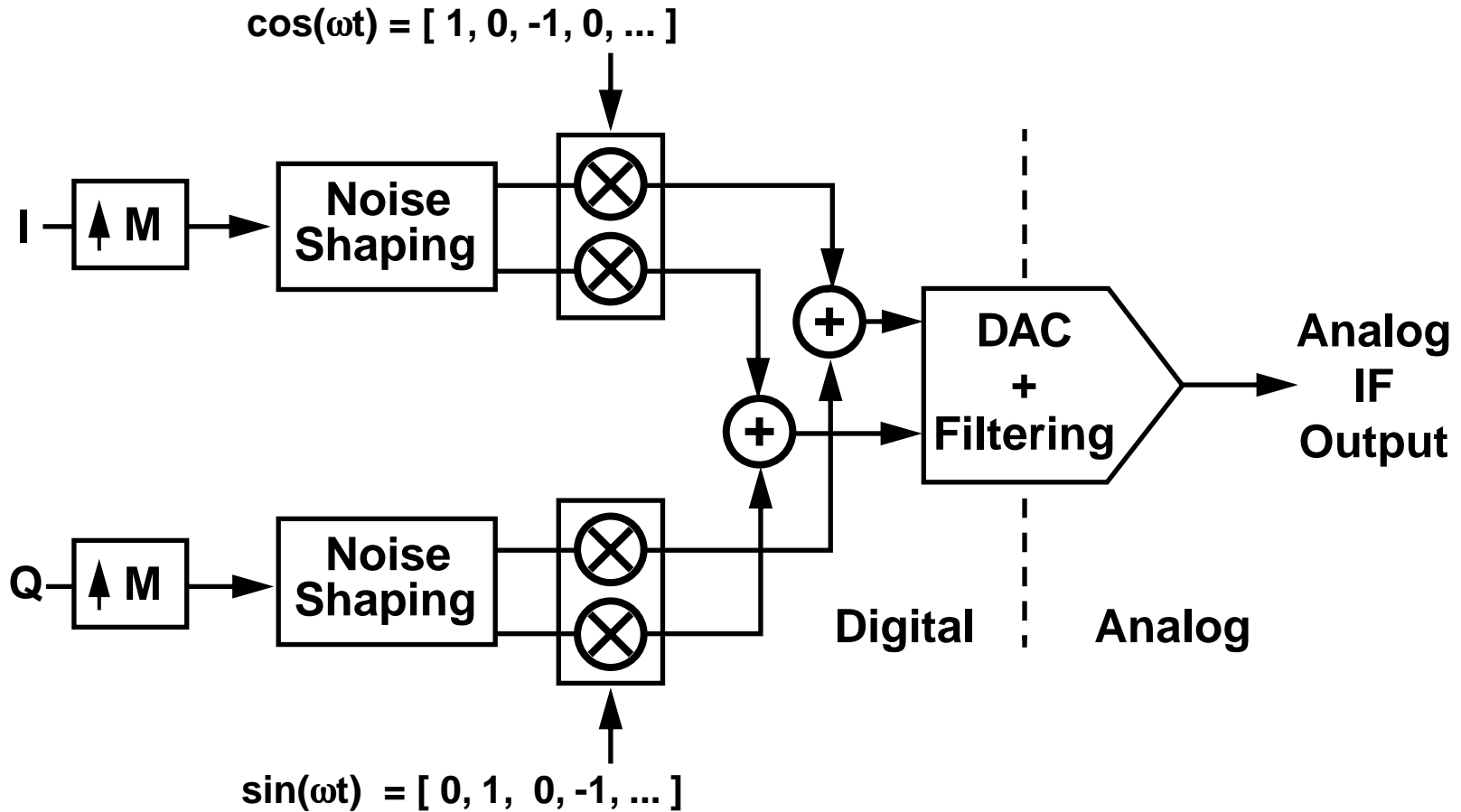


- Mix to IF (at $f_s/4$) following cascaded noise shapers
- Error cancellation performed at IF

Lowpass Cascaded Noise Shaping

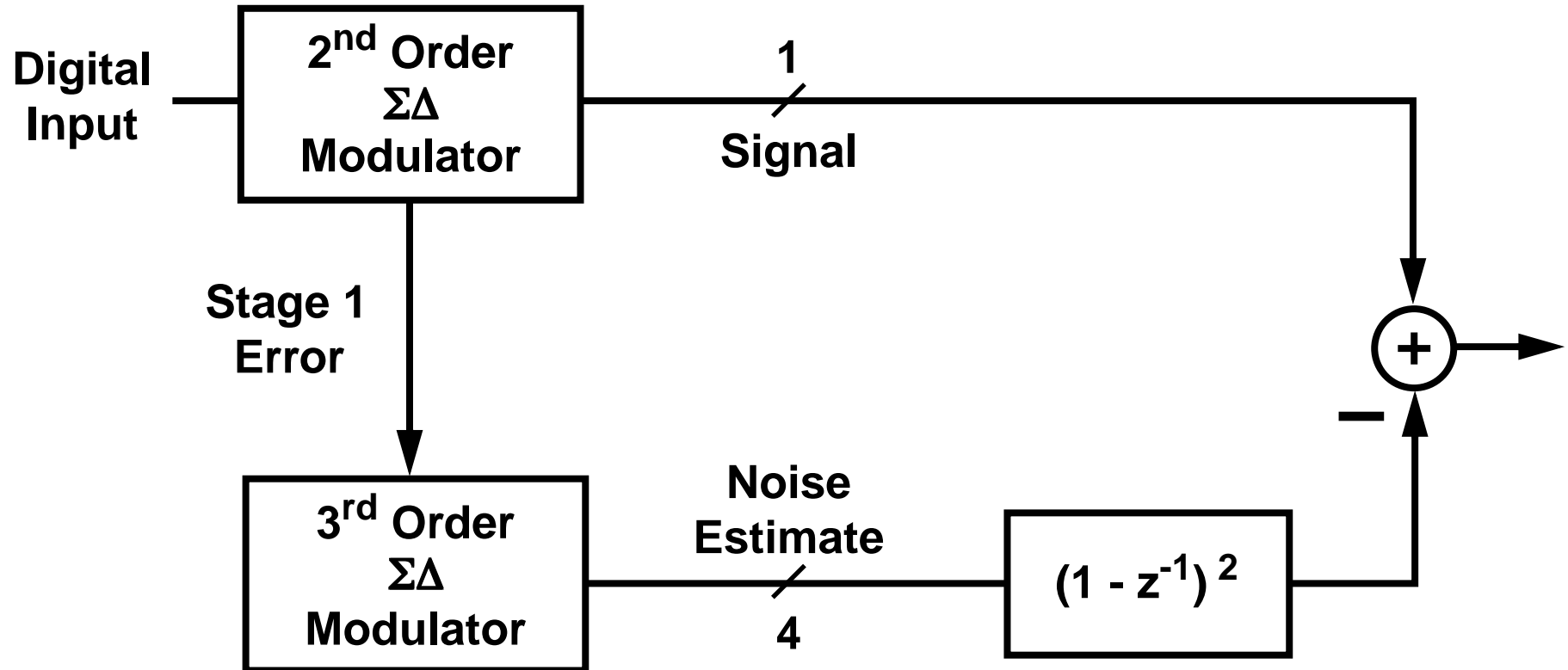


- **2nd order differentiator matches noise shaping in first stage**

DAC Architecture

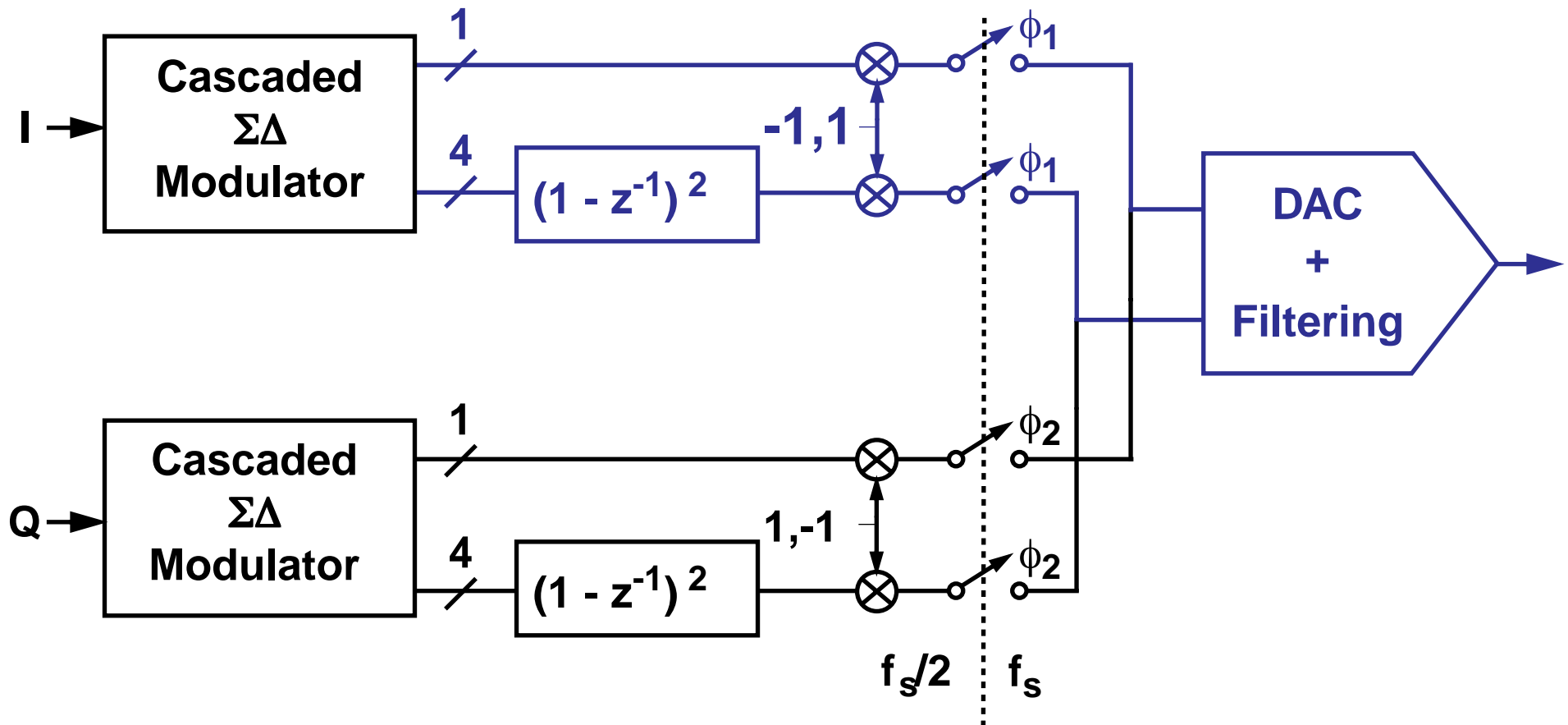


- I & Q modulators operate at $f_s/2$, saving power

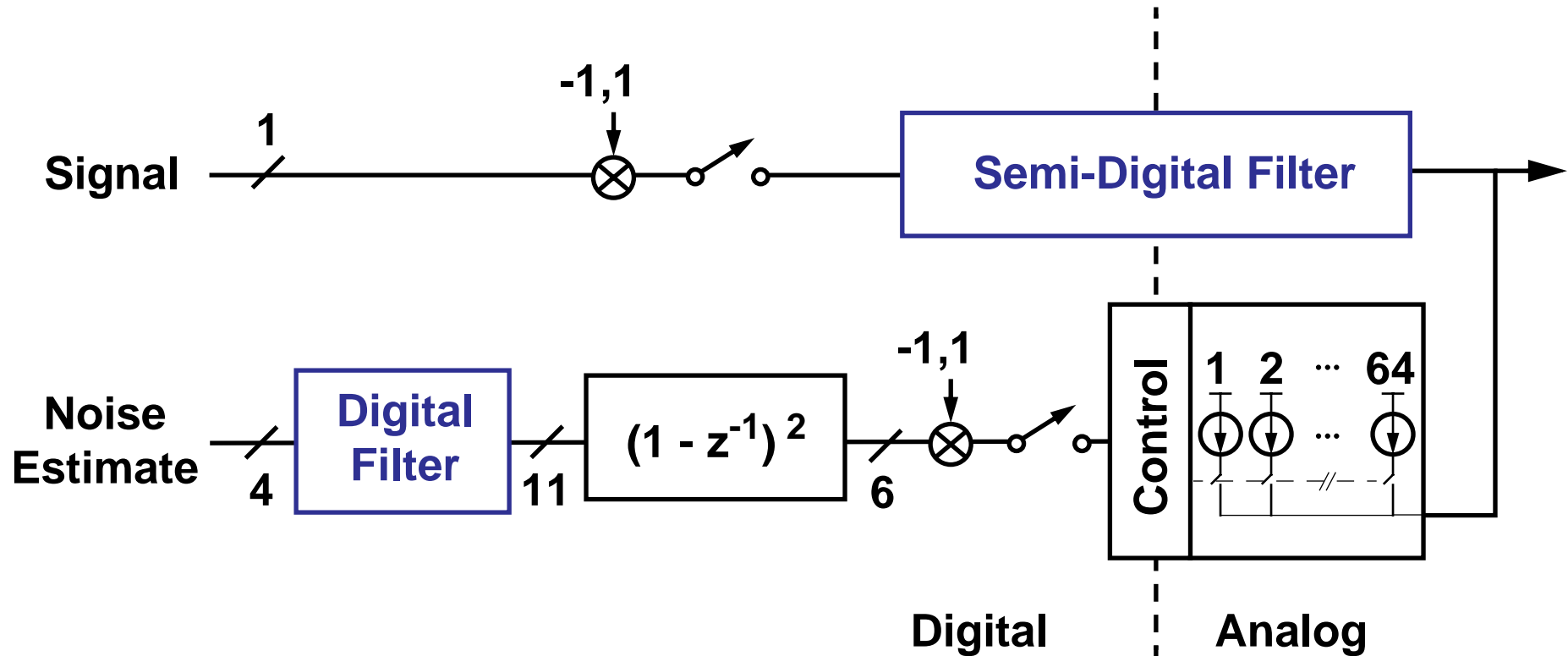Discrete Time – Continuous Time Interface



- Semi-digital filtering for reconstruction of signal
- Digital filter reduces out-of-band quantization noise
- Digital filter transfer function matches that of semi-digital filter


Semi-Digital Filter *

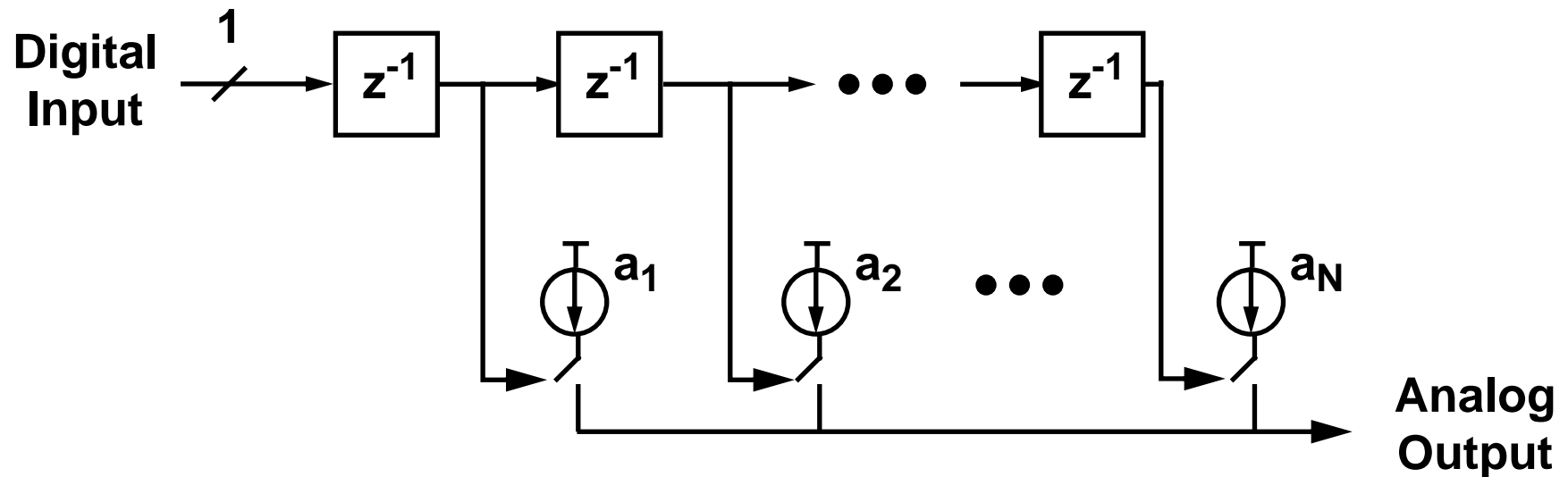


- Mismatch among current sources alters the transfer function but doesn't introduce nonlinearity
- Area limits number of taps and precision of coefficients
- Good for 1-bit signal path but not multi-bit noise estimation path

* D.Su, et al., JSSC, 1993


Bandpass Data Weighted Averaging

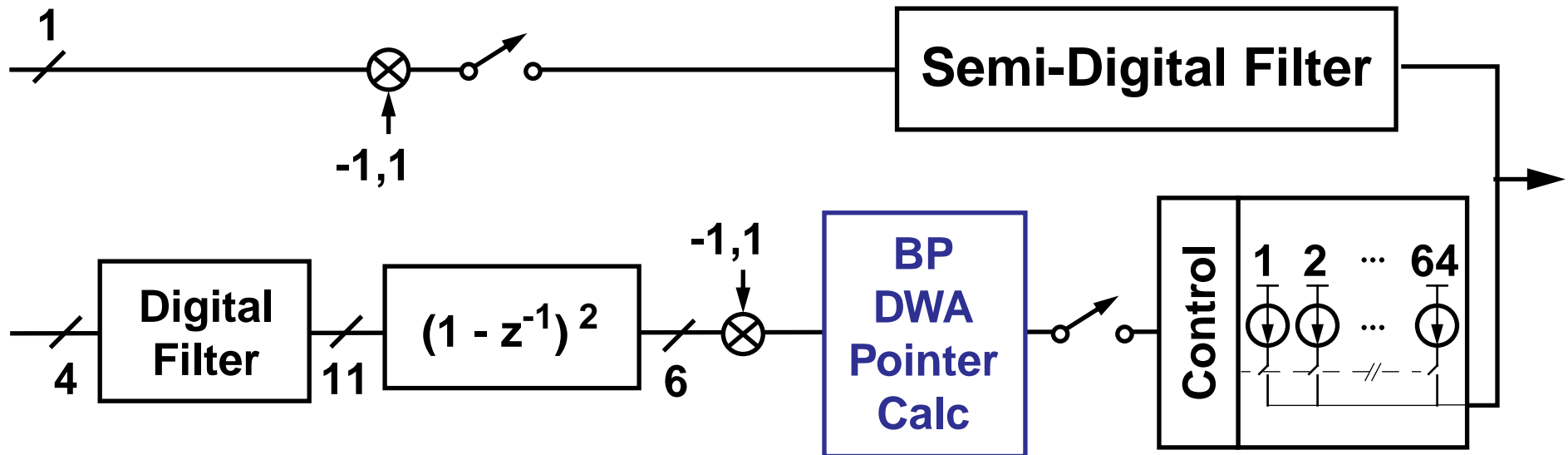

$f_s/2$ Notch

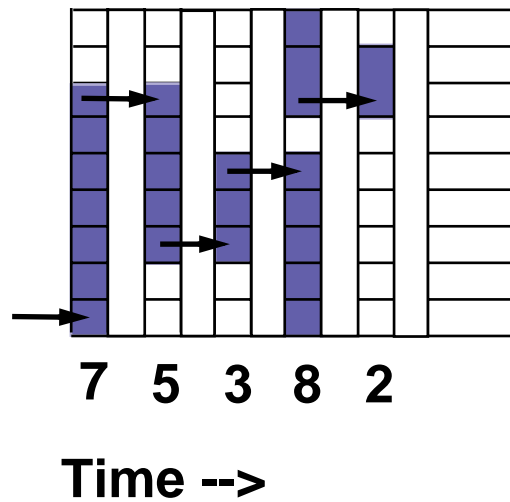


$f_s/4$ Notch

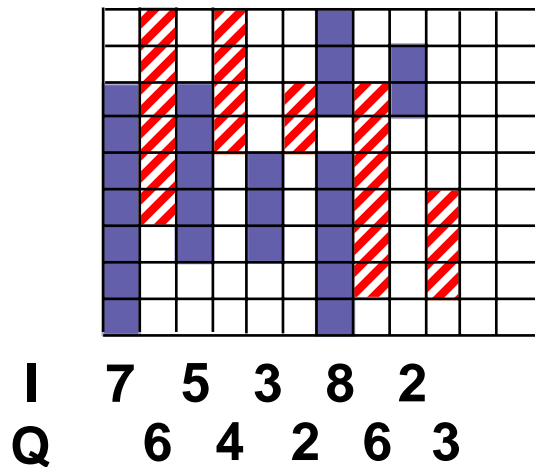


- I & Q pointer calculations are independent

* T. Shui, et al., ISCAS, 1998


Bandpass DAC Die Photo

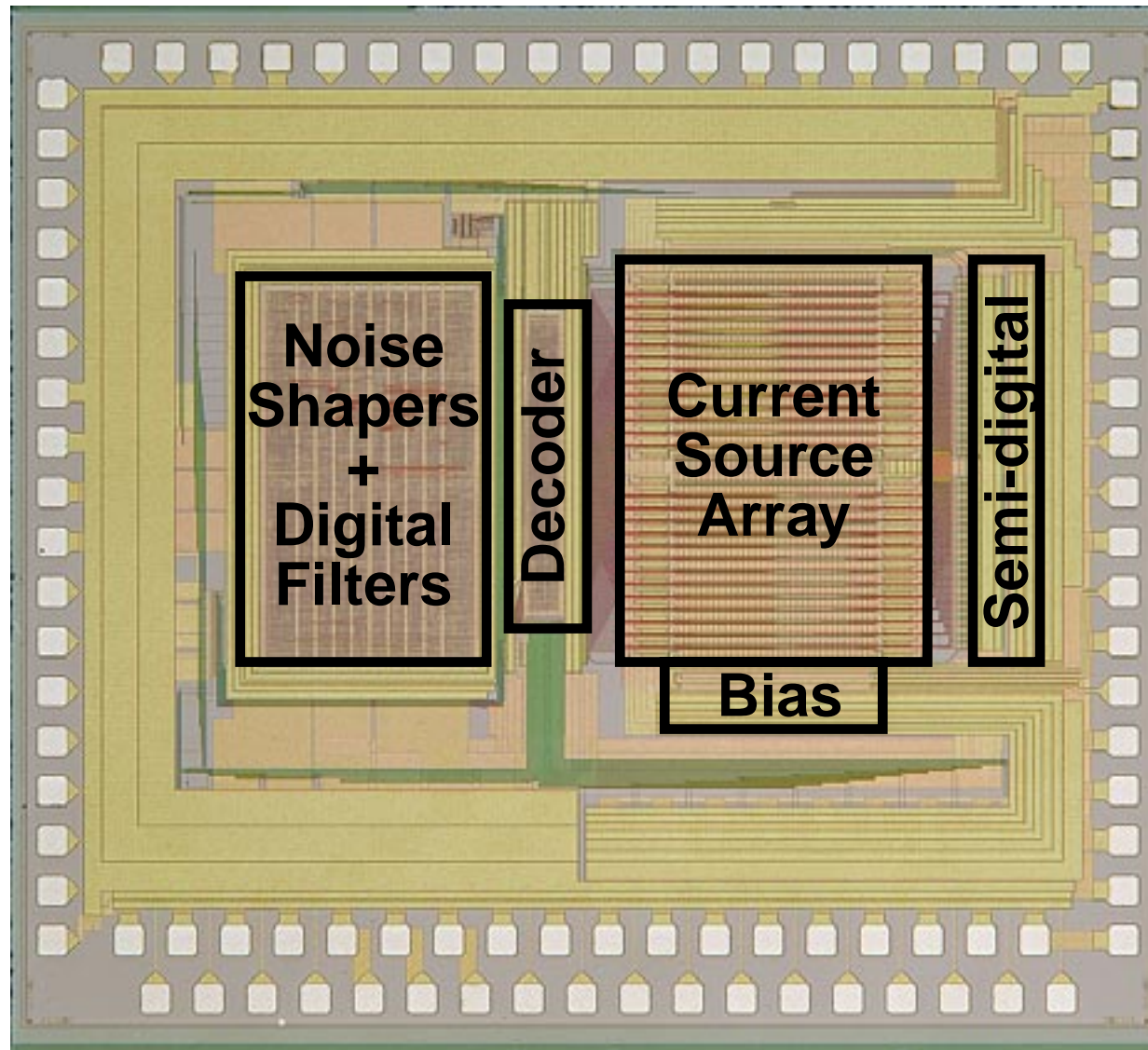

DAC Output Spectrum

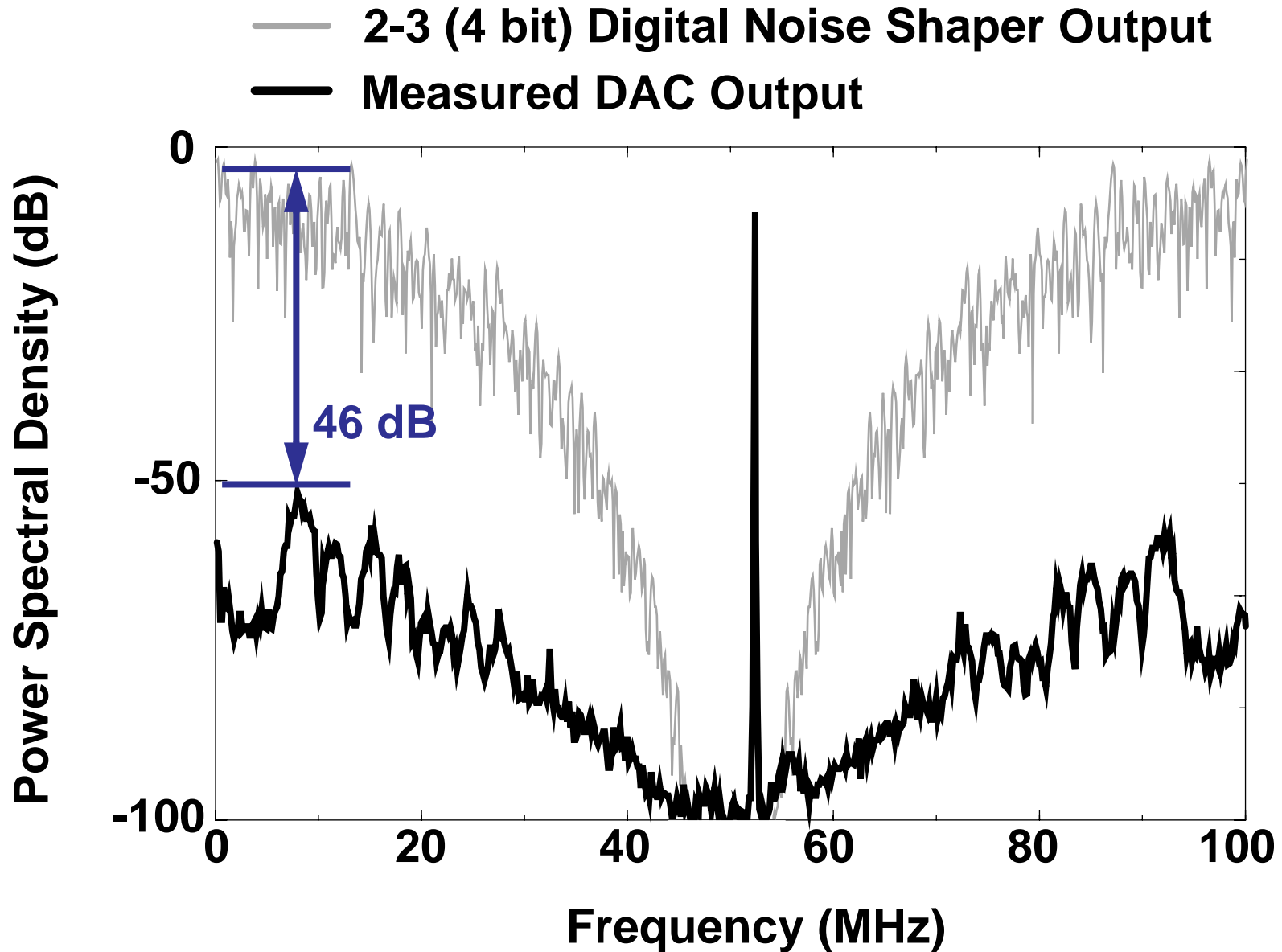

SNDR and SFDR

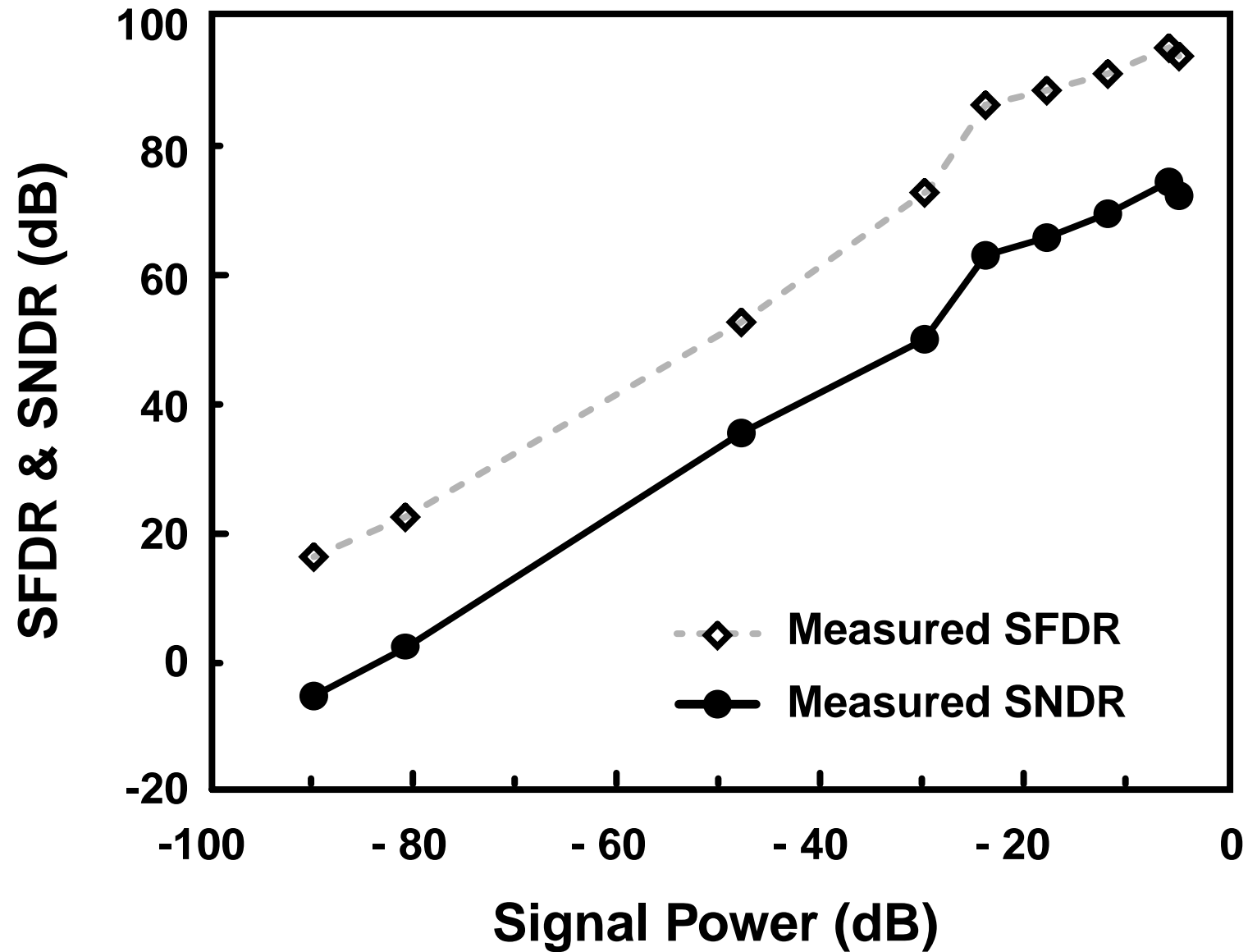

DAC Performance

Technology	1-p, 5-m 0.25-μm CMOS
Supply: Modulators and Filters Other	1.5 V 2.5 V
Center Frequency	50 MHz
Bandwidth	6.25MHz
Peak SNDR	76 dB
Dynamic Range	85 dB
Peak Out-of-Band Noise Suppression	46 dB
Mirror for -6dB input	90 dB down
Active Area	2.1 mm²
Power: Modulators and Filters Thermometer Decoders Current Source Array	30 mW 70 mW 115 mW

Summary

- **Cascades of first- and second-order noise-shaping modulator stages can be used for**
 - **A/D and D/A conversion**
 - **lowpass and bandpass data conversion**
 - **dynamic range enhancement at low oversampling ratios**
- **If properly designed, advantages include**
 - **no potential instability**
 - **decorrelation of quantization noise and input**
 - **low sensitivity to analog precision**

What's ahead?

- **Challenges in data conversion interface design**
 - **Impact of technology scaling on analog; ITRS presents problems w.r.t. leakage, output resistance and gain**
 - **Demand for increased performance driven by increased use of digital signal processing**
 - **Still room for innovation in architecture and circuits**
- **Some ongoing research**
 - **Very low voltage ($V_{DD} \leq 1.2V$) oversampling A/D and D/A conversion**
 - **Oversampling D/A conversion for DSL**
 - **Continuous-time oversampling modulators for broadband applications**